






First YEAR

# Fundamentals of Electrical Engineering

By

Dr. Eman Ahmed Awad Megahed

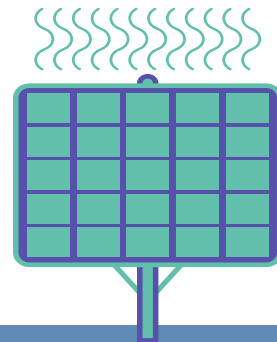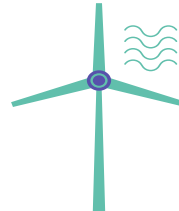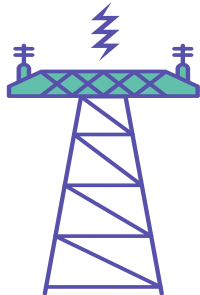

# Inductor and Inductance

## Chapter 7


# Chapter Content

## CH7: Inductor and Inductance

- 1 MAGNETIC FLUX**
- 2 INDUCTANCE AND INDUCTOR**
- 3 ENERGY STORAGE**
- 4 TOTAL INDUCTANCE**
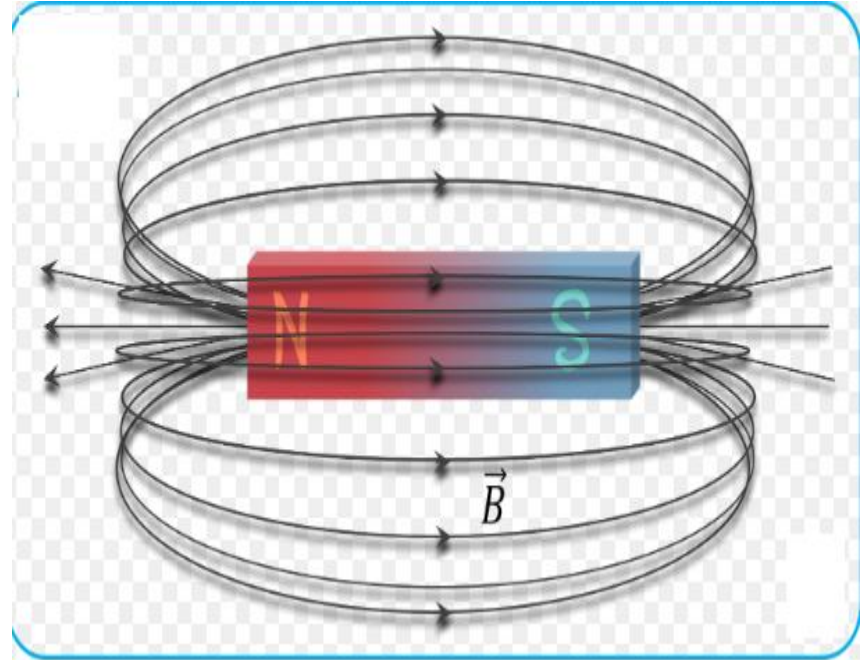
# MAGNETIC FLUX

- ❑ Magnetic phenomena are explained using magnetic flux, or just flux, which relates to magnetic lines of force that, for a magnet, extend in continuous lines from the magnetic north pole to the south pole outside the magnet and from the south pole to the north pole inside the magnet.
- ❑ The SI unit of flux is the **Weber**, with unit symbol (Wb).



## 2. INDUCTANCE AND INDUCTOR

❑ **Inductor:** is an electrical component formed by a coil of a wire



Air Core Inductor



Iron Core Inductor



Ferrite Core Inductor



Variable Core Inductor



## 2. INDUCTANCE AND INDUCTOR

- ❑ A current through the coil produces an electromagnetic field.
- ❑ When the current changes, the electromagnetic field also changes.
- ❑ The change of electromagnetic field causes an induced voltage across the coil in a direction to oppose the change of current.

$$e = - N . (d\phi / dt)$$

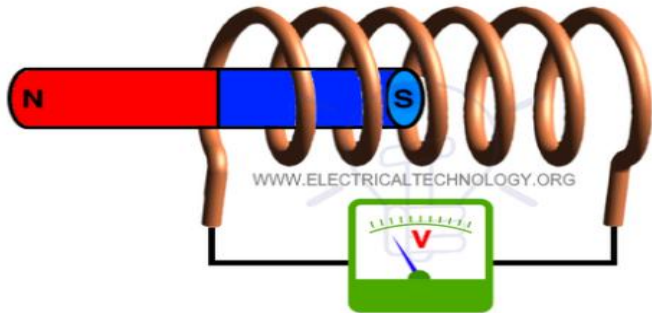


Fig 1.A: As magnet moves to the right, magnetic field is changing with respect to the coil, and EMF is induced.

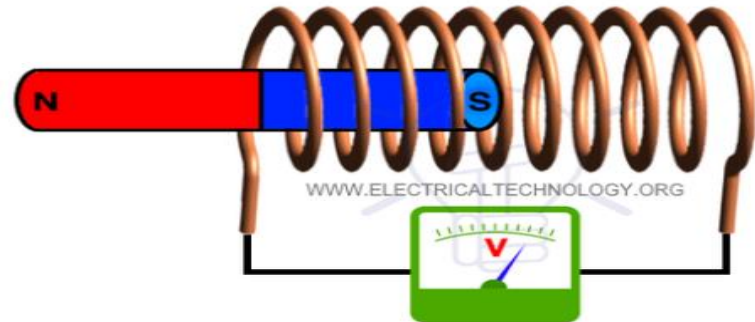


Fig 1.B: As magnet moves more rapidly to the right, magnetic field is changing more rapidly with respect to the coil and a greater EMF is induced.

## 2. INDUCTANCE AND INDUCTOR

- ❑ For most coils, a current  $i$  produces a flux linkage  $N\Phi$  that is proportional to  $I$ .


$$I \propto N\Phi$$

$$I = (1/L) N\Phi = N\Phi / L$$

$$L = N\Phi / I$$

The constant of proportionality  $L$  that is the inductance of the coil.

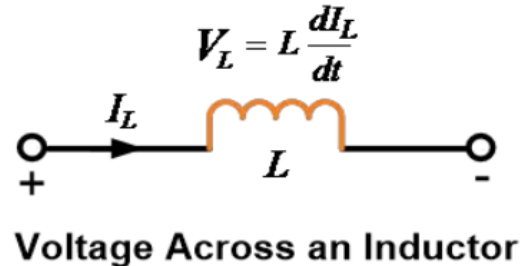- ❑ The voltage across an inductor is directly proportional to the rate of change of the electric current flowing through the inductor.
- ❑ Mathematically, the voltage across the inductor can be expressed as:  $v_L = L \frac{di_L}{dt}$



## 2. INDUCTANCE AND INDUCTOR

- ❑ **EX:** Find the voltage induced in a 150-mH coil when the current is constant at 4 A. Also, find the voltage when the current is changing at a rate of 4 A/s.

SOL:

If the current is constant,  $di/dt = 0$  and so the coil voltage is zero. For a rate of change of  $di/dt = 4 \text{ A/s}$

$$v = L \frac{di}{dt} = (150 \times 10^{-3})(4) = 0.6 \text{ V}$$



# Permeability

- ❑ **Permeability**, with quantity symbol  $\mu$ , is *a measure of this flux-enhancing property*.
- ❑ It has an SI unit of henry per meter and a unit symbol of **H/m**.
- ❑ Henry, with unit symbol H, is the SI unit of inductance.
- ❑ The permeability of vacuum, designated by  $\mu_0$ , is  $0.4\pi \mu\text{H/m}$ .
- ❑ Permeability of other materials are related to that of vacuum by a factor called the relative Permeability, with symbol  $\mu_r$

$$\mu = \mu_0 \mu_r$$


- ❑ **Most materials have relative permeability close to 1.**
- ❑ Pure iron has them in the range of 6000 to 8000.
- ❑ Nickel has them in the range of 400 to 1000.
- ❑ Alloys السبائك has a relative permeability of over 80 000.

## 2. INDUCTANCE AND INDUCTOR

- ❑ The inductance of a coil depends on the shape of the coil ( $A$ ,  $L$ ), the permeability of the surrounding material ( $\mu$ ), the number of turns ( $N$ ), the spacing of the turns, and other factors.

$$L = N^2 \cdot \mu \cdot A / l$$

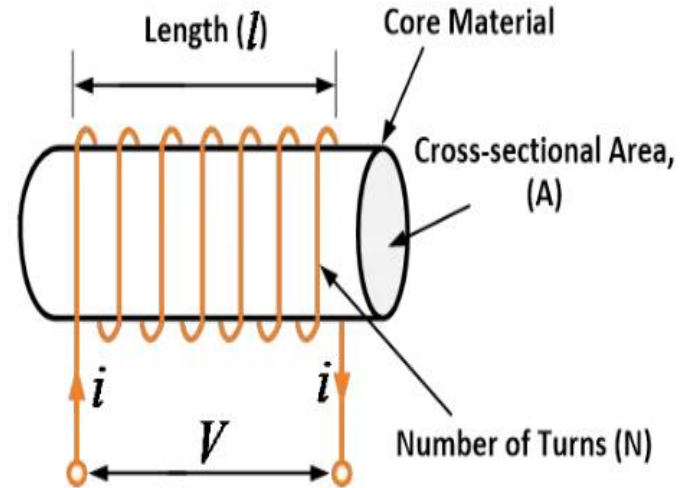where  $N$  is the number of turns of wire,  $A$  is the core cross-sectional area in square meters,  $l$  is the coil length in meters, and  $\mu$  is the core permeability.



### 3. ENERGY STORAGE

- ❑ The energy stored in an inductor is:  $W_L = \frac{1}{2} LI^2$

where W is in joules, L is in Henrys, and I is in Amperes.

- ❑ This energy is considered to be stored in the magnetic field surrounding the inductor.

## 4.TOTAL INDUCTANCE

- ❑ the current is same in all three inductors,

$$I_1 = I_2 = I_3$$

- ❑ Also, we know that the voltage through :  
inductor is given by  $V = L (di/dt)$


$$V = V_{L1} + V_{L2} + V_{L3}$$

$$L_T \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

*Series Inductances*

$$L_{\text{total}} = L_1 + L_2 + \dots L_n$$

Inductors in Series

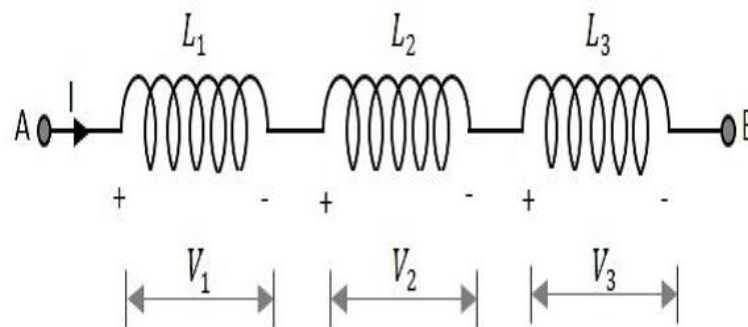

## 4. TOTAL INDUCTANCE

- the Voltage is same in all three inductors,


$$V_1 = V_2 = V_3$$

- Also, we know that the voltage through an inductor is given by  $V = L (di/dt)$

$$I = I_1 + I_2 + I_3$$

$$v = L_T \frac{d}{dt} (i_1 + i_2 + i_3) = L_T \left( \frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} \right)$$
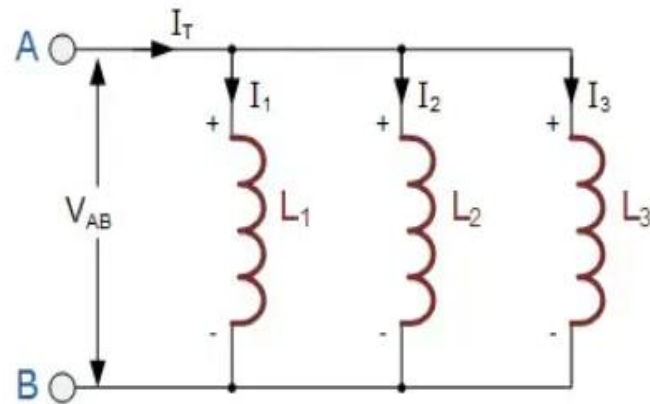
$$v = L_T \left( \frac{v}{L_1} + \frac{v}{L_2} + \frac{v}{L_3} \right)$$



*Parallel Inductances*

$$L_{\text{total}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}}$$

# ENERGY STORAGE

**EX:** Find the total inductance of three parallel inductors having inductances of 45, 60, and 75 mH.

SOL:

$$L_T = \frac{1}{\frac{1}{45} + \frac{1}{60} + \frac{1}{75}} = 19.1 \text{ mH}$$

# End of Lecture 9

