

## Capacitors:-

- Two conductor separated by an insulator
- Store electric charge with (+) on one conductor and (-) on the other


→ symbol:  C (F)

→ Capacitance: ability of capacitor to store charge

$$C = \frac{Q}{V} \quad \leftarrow \begin{array}{l} \text{Charge (C)} \\ \text{Potential difference between two conductors} \end{array}$$

C → F (Farad) (MF, mF)

$$C = \epsilon \frac{A}{d} \quad \leftarrow \begin{array}{l} \text{Area of either plate (m}^2\text{)} \\ \text{Permittivity} \quad d \leftarrow \text{separation (m)} \end{array}$$

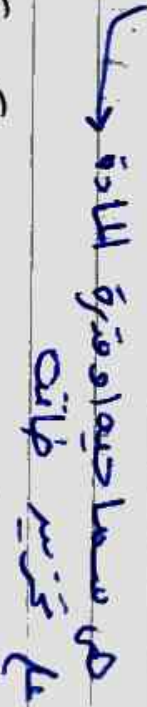(F/m) → 

$$\epsilon = \epsilon_0 \epsilon_r$$

→ Permittivity of vacuum (8.85 pF)

$\epsilon_r \rightarrow$  air 1.0006

paraffine paper 2.5

mica 5

glass 7.5

mica 7500

total Capacitance  $\text{المساحة الكلية}$  \*

Parallel  $C_T = C_1 + C_2 + C_3 + \dots$


Series  $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$

Energy storage  $W_e = \frac{1}{2} C V^2$   
 $\frac{1}{2} \text{ Volt}$

inductor:

- \* Passive electrical component
- \* Stores energy in magnetic field when electric current flows through it

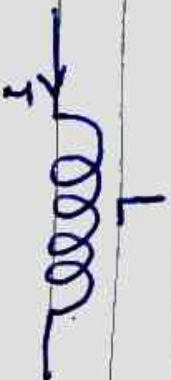Flux  $\Phi$  (wb)  $\text{المجال}$   
 Flux density (B)  $\text{كثافة المجال}$





في الدوائر

المعادلات

$$L_i = N \Phi \rightarrow \text{Linkage Flux}$$

inductance (H)

$$L = \frac{N \Phi}{I} \leftarrow \text{Current}$$

Gross section Area (m<sup>2</sup>)

$$L = \frac{N^2 \mu}{l} \frac{A}{l} \leftarrow \text{length (m)}$$

Permeability

$$\mu = \mu_0 \mu_r$$

↳ Permeability of vacuum ( $4\pi \times 10^{-7}$ ) H/m

في الدوائر المتعددة

$$\text{induced voltage} \quad (e) \quad e = \frac{N d \Phi}{dt} = L \frac{di}{dt}$$

Total inductance  $L_T$  series

$$L_T = L_1 + L_2 + L_3 + \dots$$

Parallel

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$$

Energy Storage


$$W_L = \frac{1}{2} L i^2$$

سيد العالين


Sec (7) 325

Lab (3) Thevenin Equivalent Circuit

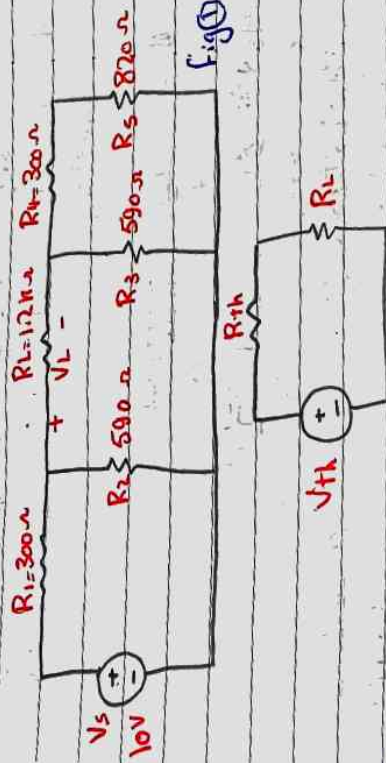**objective:-** verify Thevenin's Theorem by obtaining Thevenin equivalent Voltage  $V_{th}$  and Thevenin Equivalent resistance  $R_{th}$  for the given circuit.



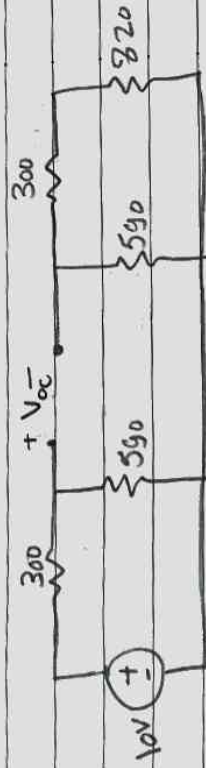① معزول وبقس الاجه R1 وسجل قلة ال  
② لا دقيه ال هزف الغا و R1  
وخل محال open وبقس صعه و R1 ال




note  $V_{th}$  is The voltage on 590 n

ಇವು

الموضوع :-

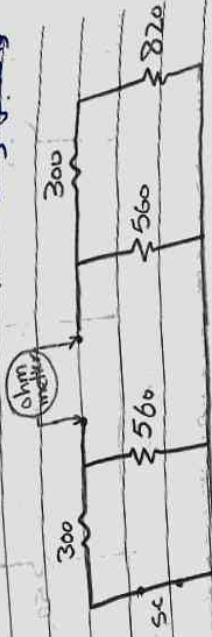scantigogine Rth qüçplür bir jekt geline ③  
Rth öcölgeles



٥) اوجد محاسن  $T_{\text{Jensen}}$  واصعب قيده  $R_{\text{L}}$  على  $R_{\text{H}}$   
 $R_{\text{H}} = 585,31$   
 مستوى القيادة اللا وني  $\alpha = 5\%$



$V_{th} = 6.5 \text{ u.c.}$   $R_{th} = 594 \Omega$   $V_L$  couple




Ex) Fig 1 by using Thevenin Theorem find  $V_L$



Fig 1

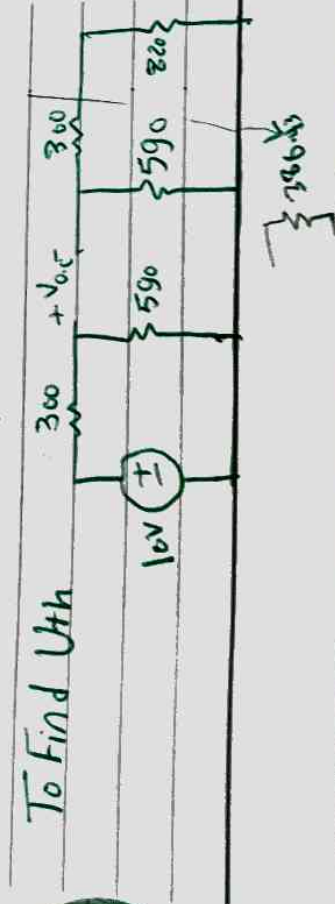- خطوات الحل (1) حذف  $R_L$  وإعطاء مكانه مفتوح open
- (2) فرض المقاومة المكافئة من جهة المصدر open s.c
- المقاومة المقادير الغير معتمدة بتحويل مصدر الجهد الى مصدر تيار  $I_N$
- (3) مخرج المصدر تانين وإعطي وجهه الى open للحصول على  $V_{Th}$
- (4) فرض مكان  $V_{Th}$  (Thevenin Voltage) على التوالي  $R_L$
- وإيجاد قيمة  $V_L$  أو التيار  $I_L$  على  $R_L$



To Find  $V_{Th}$

To find  $R_{Th}$

$$\left( \frac{300 \parallel 590 \right) = 198.876$$

$$\left( 300 + 820 \right) = 1120$$

$$1120 \parallel 590 = 386.43$$

$$R_{Th} = 198.876 + 386.43 = 585.31$$

التاريخ:

الموضوع:



by using Voltage divider


المقاومة القوية (590)

$$V_{Th} = 10 \times \frac{590}{300 + 590} = 6.6 \text{ V}$$

جمع المقادير


Thevenin equivalent Circuit

$V_L$  by using Voltage divider is

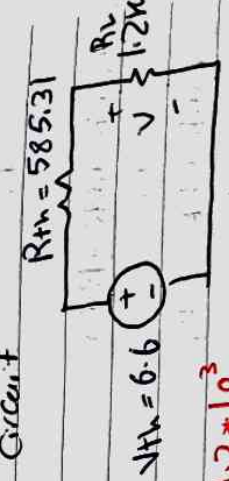


$$V_L = 6.6 \times \frac{1.2 \times 10^3}{1.2 \times 10^3 + 585.31} = 4.4 \text{ volt}$$

# Delta - Star Transformation

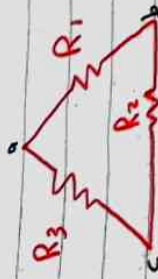

شبكة دلتا

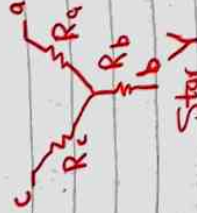

شبكة نجمة

Y-D

المركبة



D-Y


$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

المركبة


$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

Ex

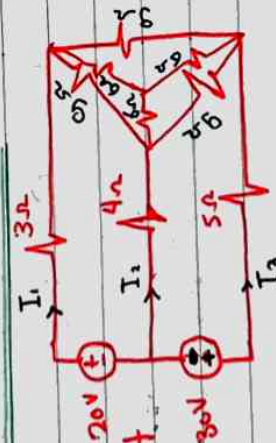

Find indicated Current in The Circuit

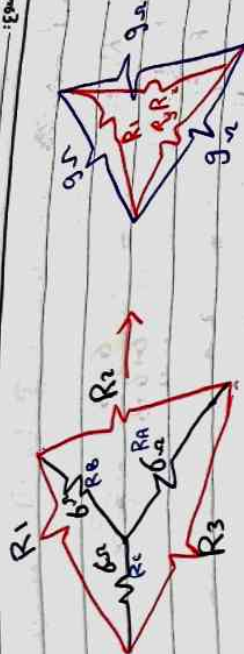


Y → Δ

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} = \frac{6 \times 6 + 6 \times 6 + 6 \times 6}{6} = 18 \Omega$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} = 18 \Omega$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b} = 18 \Omega$$

$$18 \Omega // 9 \Omega = 6 \Omega$$

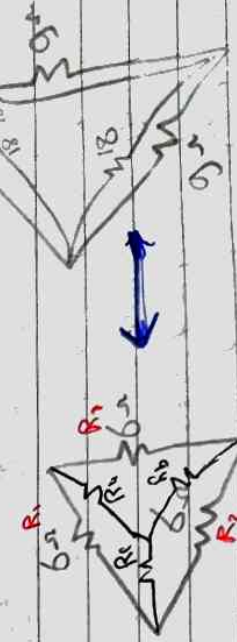







## LAB (4) Norton Equivalent Circuit

**Objective:** - Verify Norton theorem by obtaining The Norton equivalent circuit ( $I_N$ ,  $R_N$ )

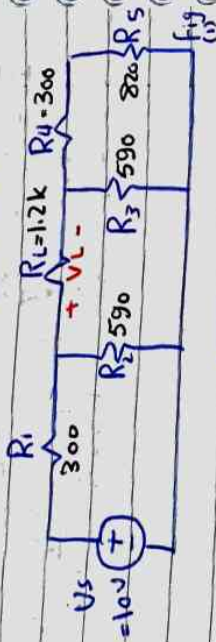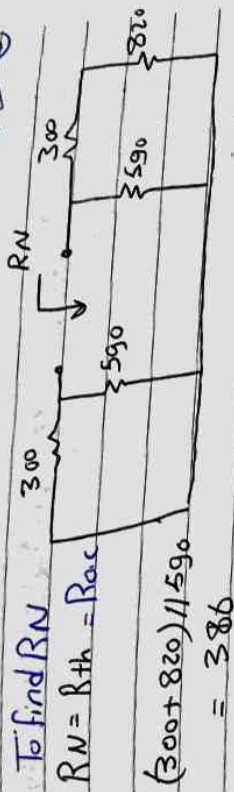**Procedure:**

- Construct the circuit as shown in Fig (1)
- Measure the voltage  $V_L$  across the load  $R_L$
- Find  $I_N$  by removing the load resistance and measuring the current of short circuit  $I_{SC} = I_N$
- Find  $I_N$  by removing voltage source and the load and measuring open circuit resistance
- Obtaining  $I_N$ ,  $R_N$  as shown in Fig (2)
- Measure the current on  $R_L \rightarrow V_L$

قنوات حل دوائر Norton  
 (1) احذف  $R_L$  وادخل سلك open circuit  
 (2) ادفق المالحظ ( $I_{SC}$ ) كتيار (س.ك)  
 (3) احسب  $R_N$  مكان الدائرة short  
 (4) ارجع المالحظاتي واحسب التيار الى هبة في الدائرة  
 هكذا المالحظ  $I_N = I_{SC}$   
 (5) اوجد مكان Norton واحسب التيار الى هبة في الدائرة



$$R_N = R_{th} = R_{ac}$$

$$(300 + 820) \parallel 590$$

$$= 386$$

$$300 \parallel 590 = 198$$

$$R_N = 386 + 198 = 584 \Omega$$

to find  $I_N$ 

$$I_N = I_{SC}$$

by using mesh

$$10 - 300 I_1 - 590 (I_1 - I_2) = 0$$

$$+ 890 I_1 - 590 I_2 = 10 \rightarrow (1)$$

$$- 590 (I_2 - I_1) - 386 I_2 = 0 \rightarrow (2)$$

$$590 I_1 - 976 I_2 = 0$$

$$I_1 = 0.0187 A$$

$$I_2 = 0.0113 A$$

$$I_{SC} = I_2 = 0.0113 A$$


$$I_1 = 0.0187 A$$

$$I_2 = 0.0113 A$$

$$I_{SC} = I_2 = 0.0113 A$$



# Norton equivalent circuit

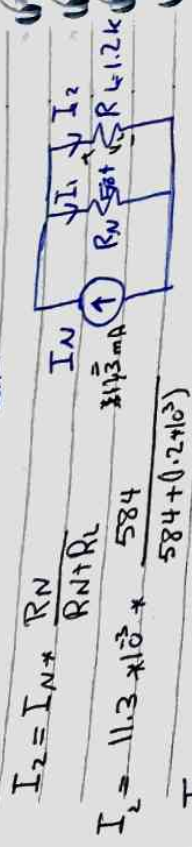

$$I_2 = I_N \times \frac{R_N}{R_N + R_L} = 11.3 \times 10^{-3} \times \frac{584}{584 + (1.2 \times 10^3)} = 3.699 \text{ mA}$$

$$V_L = I_2 R_L = 3.699 \times 10^{-3} \times 1.2 \times 10^3 = 4.4 \text{ V}$$

## النتيجة

$V_L$ الجهد الكلي	4.4 V
$R_N$	584 $\Omega$
$I_N = I_{s.c}$	11.3 mA
$V_L$ الجهد الكلي	4.4 V


## Objective:-

Verify the superposition theorem.
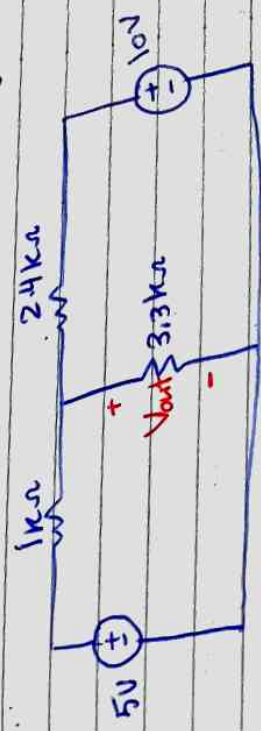
## Theory:-

In this exercise superposition theorems are examined by applying it to the circuit given below

**Superposition** states that the response in a linear circuit with multiple sources can be obtained by applying adding the individual responses caused by separate independent source acting alone for an independent source acting alone all other voltage are replaced by short circuits and all independent current source are replaced by open circuit




## Procedure

- ① Construct the circuit fig ①
- ② measure voltage at  $3.3k\Omega$  (Vout)
- ③ remove 5 volt and replace it by short circuit as fig ②
- ④ measure Vout' at  $3.3k\Omega$
- ⑤ replace 10 volt by short circuit as fig ③
- ⑥ measure Vout'' at  $3.3k\Omega$
- ⑦ Calculate the total response (Vout) for circuit by adding the response from fig ②, fig ③

$$V_{out} = 0.88 \times 10^{-3} \times 3.3 \times 10^3 = 2.9 \text{ Volt}$$

$$V_{out}' = 3 \times 157 \times 10^{-3} \times 3.3 \times 10^3 = 10.4 \text{ Volt}$$

$$V_{out} = 12.3 \text{ Volt}$$

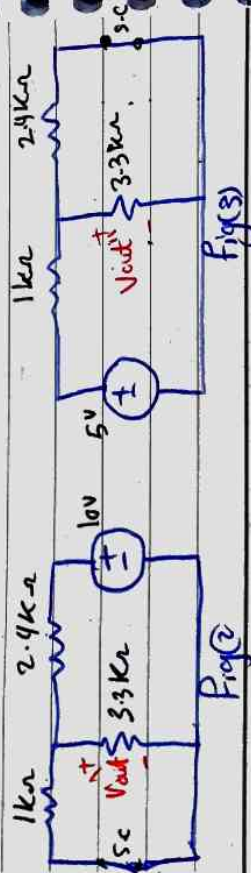

## Capacitor and inductor

### Capacitors:-

- Two Conductor separated by an insulator
- Store electric charge with (-) on one conductor and (+) on the other
- symbol:  $\parallel \text{C} \parallel$
- Capacitance: ability of capacitor to store charge

$$C = \frac{Q}{V} \quad \leftarrow \begin{array}{l} \text{Charge} \\ \text{Potential difference between two conductors} \end{array}$$

$$C \rightarrow F \text{ (Farad)} \quad (\mu F, mF)$$

$$C = \epsilon \frac{A}{d} \quad \leftarrow \begin{array}{l} \text{Permittivity} \\ \text{Area of either plate (m}^2\text{)} \\ \text{d} \leftarrow \text{separation (m)} \end{array}$$

في سعة المكثف  $\rightarrow$   $\epsilon = \epsilon_0 \epsilon_r$

$$\epsilon = \epsilon_0 \epsilon_r$$

Permittivity of vacuum  $(8.85 \times 10^{-12})$

$\epsilon_r \rightarrow$	air	1.0006
	paraffine paper	2.5
	mica	5
	glass	7.5
	mica	4500



total Capacitance عكس المقاومة \*

Parallel  $C_T = C_1 + C_2 + C_3 + \dots$


Series  $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$

Energy storage  $W_C = \frac{1}{2} C V^2$   $\frac{J}{F} \rightarrow \text{volt}$

inductor:

- passive electrical component
- stores energy in magnetic field when electric current flows through it

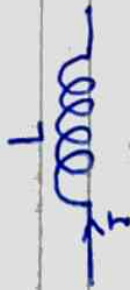Flux  $\Phi$  (wb) الفي  
Flux density (B) الفي  
نسبة



$L_i = N\Phi \rightarrow$  Linkage Flux  
inductance (H)

$L = \frac{N\Phi}{I} \leftarrow$  Current

$L = N^2 \mu \frac{A}{l} \leftarrow$  Gross section Area (m)  
Permeability  $\mu$   $\leftarrow$  Length (m)

$N = \mu_0 H$

$\rightarrow$  permeability of vacuum  $(4\pi \times 10^{-7}) \text{ H/m}$

$\mu \rightarrow$  الفي للمادة الفي

induced voltage (e)  $e = \frac{N d\Phi}{dt} = L \frac{di}{dt}$

Total inductance  $\mu_0 \mu_r \mu_0 / \mu$

Series

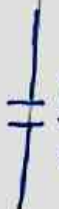

$L_T = L_1 + L_2 + L_3 + \dots$

Parallel

$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$

Energy Storage

$W_L = \frac{1}{2} L i^2$

Symbol	Capacitor	inductor
	 C (F)	 L (H)
Calculation	$C = \frac{Q}{V}$ $C = \epsilon \frac{A}{d}$	$L = \frac{N\Phi}{i}$ $L = N^2 \mu \frac{A}{l}$
	Permeability $\epsilon = \epsilon_0 \epsilon_r$ $\epsilon_0 = 8.85 \text{ pF/m}$ $\epsilon_r \rightarrow$ متغيرا خلافا للواحد	Permeability $\mu = \mu_0 \mu_r$ $\mu_0 = 4\pi \times 10^{-7} \text{ (H/m)}$ $\mu_r \rightarrow$ متغيرا خلافا للواحد
total		
Series	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$	$L_T = L_1 + L_2 + L_3 + \dots$
Total		
Parallel	$C_T = C_1 + C_2 + C_3 + \dots$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$
Energy Storage	$W_C = \frac{1}{2} C V^2$ (J)	$W_L = \frac{1}{2} L i^2$ (J)