


أسس الهندسة الإلكترونية

Ministry of Higher Education		
Manzala Higher Institute for Engineering and Technology		
First semester : 2021/2022		Date: 16/1/2022
Final Exam		Level: 1
Department: Electronic Engineering		Time allowed: 3 hrs.
Total Marks: 90		Code: COM113
Course title: Fundamentals of Electronic Engineering		Examiner: Dr. Mohamed Abdel Rahman

Answer the Following Questions:

Question (1):

(Total marks: 20)

- a) Aided with the configurations, sketch a center-tapped transformer circuit for a full wave rectifier and demonstrate the output voltage in case of with and without capacitor filter. (10 marks)

- b) A 15V - 0 - 15V (rms), 50 Hz, an ideal center-tapped transformer, is used with FWR circuit with diodes having voltage drop 1V, capacitor $C = 10000 \mu F$ is applied as a filter capacitor across the load resistance $R_L = 100 \Omega$, Determine the following: (10 marks)

- i) DC load current I_{DC} . ii) DC load voltage E_{DC} . iii) Ripple factor γ .

Question (2):

(Total marks: 25)

- a) Draw the equivalent circuit of the practical model for the photovoltaic solar cell using a single diode model and define its parameters in detail. Also write down the equations describing this model. (9 marks)

- b) Consider a zener diode regulator circuit as shown in Fig. 1. $V_{SS} = 24\text{ V}$, $R = 1.2\text{ k}\Omega$, $R_L = 6\text{ k}\Omega$ and $V_Z = 10\text{ V}$. Compute the following: (10 marks)

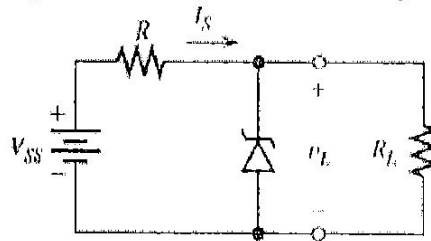


Fig.1

- i) The current flowing through the load, I_L
- ii) The source current, I_S
- ii) The zener current I_Z at full load
- iii) Power of zener diode P_Z
- iv) Power supplied by the source, P_S
- v) Output voltage with removing the zener diode

c) Compare the parameters of following two diodes.

(6 marks)

No.	Parameters	Light emitting diode (LED)	Photo diode
1	function		
2	Schematic symbol		
3	Bias for normal operation		
4	Applications (at least two)		

Question (3):

(Total marks: 20)

a) For the common emitter BJT amplifier circuit shown in Fig.2, calculate I_B , I_C , V_{CE} , V_B , V_C and V_{CB} . Also draw its ac equivalent circuit. (11 marks)

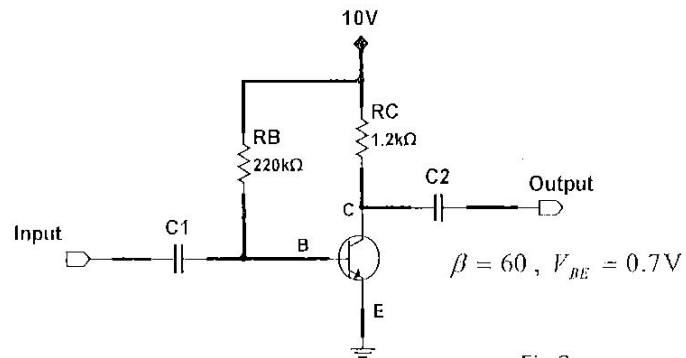


Fig.2

b) Compare the following parameters for the BJT and JFET devices.

(9 marks)

No.	Parameters	BJT	JFET
1	Control element		
2	Device type		
3	Types of carriers		
4	Input resistance		
5	Thermal noise		
6	Schematic symbol		

Question (4):

(Total marks: 25)

a) Aided with the configurations, draw the structure of both JFET and MOSFET devices.

Also discuss and explain the physical operation for each one of them.

(5 marks)

- b) Draw and explain one of the applications for the silicon-controlled rectifier (SCR).
(5 marks)

- c) A JFET shown in Fig. 3 has values of $V_{GS(off)} = -8V$ and $I_{DSS} = 16\text{ mA}$. Determine the values of V_{GS} , I_D and V_{DS} .
(5 marks)

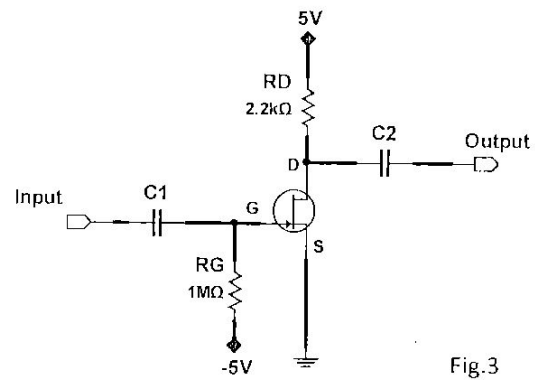


Fig.3

- d) Draw the output ($I_D - V_{DS}$) and transfer ($I_D - V_{GS}$) characteristics of the n-channel JFET and illustrate the different regions of operation. (5 marks)

- e) Tabulate the following parameters for the JFET and MOSFET devices. (5 marks)

No.	Parameters	JFET	MOSFET
1	Abbreviation represents....		
2	Modes of operations		
3	Thermal noise		
4	Susceptible to damage		
5	Input impedance		
6	Schematic symbol		

With my best wishes.