

**Ministry of Higher Education**

**Manzala Higher Institute for Engineering and Technology**

**Second semester :2023/2024.**

**Department: Electronic Eng.**

**MidTerm**



**Course title: Fundamentals Of Electrical Circuits**

**Code: COM111**

**14/11/2023**

Name/

**Answer the Following Questions:**

**Question# 1 (5 Marks)**

1- SI unit of Force is .....

- (a) Joule                      (b) Newton                      (c) Coulomb                      (d) Ampere

2- What is the current from a steady flow of 100 C through a wire cross section in 20s?

- (a) 50A                      (b) 2000A                      (c) 10A                      (d) 5A

3- What is the input power in watts to 1 hp electric motor operating at 90% efficiency?

- (a) 528W                      (b) 90 W                      (c) 829 W                      (d) 1.11 W

4- An open circuit has an ..... resistance, which means that it has zero current flow through it for any finite voltage across it.

- (a) Zero                      (b) Infinite                      (c) Small                      (d) Medium

5- "The algebraic sum of the currents leaving a closed surface is zero", is one version of ..... law

- (a) Ohm                      (b) KCL                      (c) KVL                      (d) Ampere`s

**Question# 2 (5 Marks)**

6-Using Nodal analysis, Determine the voltage at N and  $I_o$ , at Fig. 1?

**Question# 3 (5 Marks)**

7- Use Mesh analysis to find the currents in the circuit at Fig. 2?

**Question# 4 (5 Marks)**

8- Using Current divider find the currents passing in each resistor at Fig. 3?

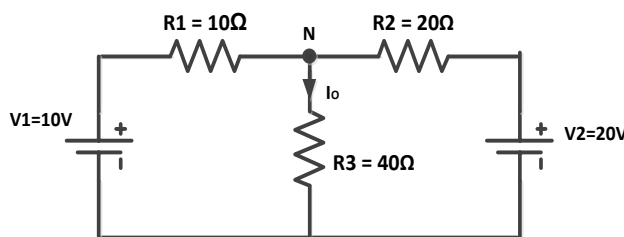


Fig 1

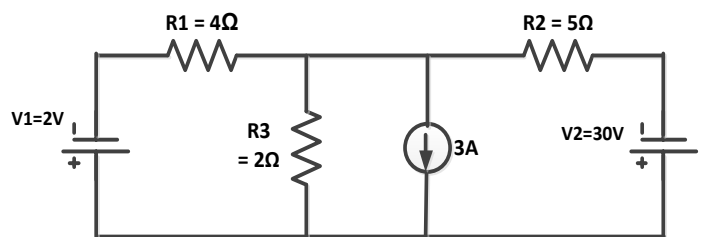


Fig 2

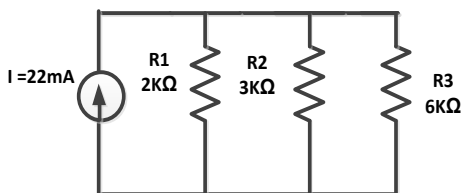


Fig 3