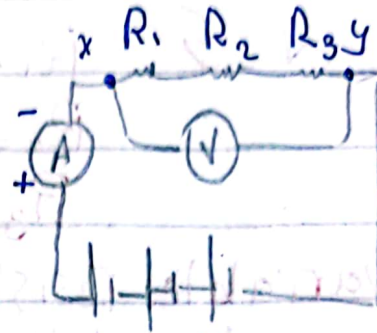


lec 3

end to end  
connected in Series




$$V = V_1 + V_2 + V_3$$

$$IR_+ = IR_1 + IR_2 + IR_3$$

$$\# R_+ = R_S = R_1 + R_2 + R_3$$

Ex:  $R_S = R_1 + R_2 = 6\Omega$

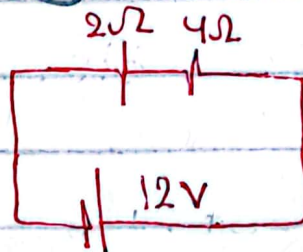
$$I_+ = \frac{V}{R_+} = \frac{12}{6} = 2A$$



$$V_1 = IR_1 = 2 \times 2 = 4V$$

$$V_2 = IR_2 = 2 \times 4 = 8V$$

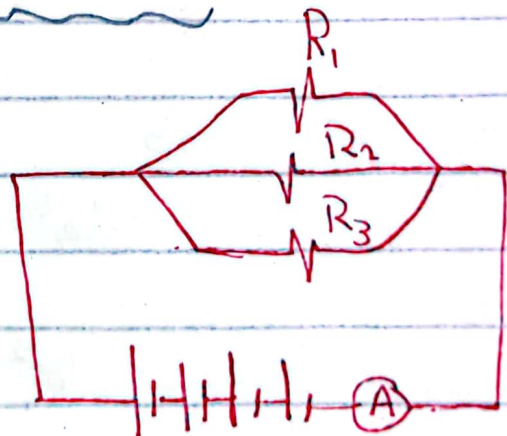connected together  
between x, y  
"parallel"



$$I = I_1 + I_2 + I_3$$

$$\frac{VS}{R_P} = \frac{VS}{R_1} + \frac{VS}{R_2} + \frac{VS}{R_3}$$




$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$2R \rightarrow R_t = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$\frac{1}{R_{p1}} = \frac{1}{12} + \frac{1}{6} + \frac{1}{4}$$

$$= 0.5$$


$$R_1 = 2$$

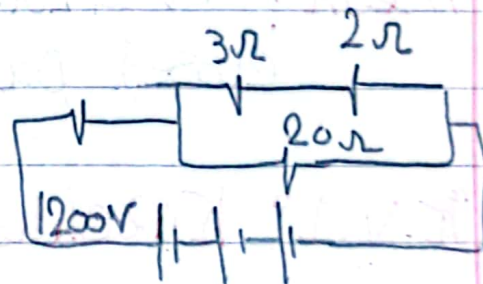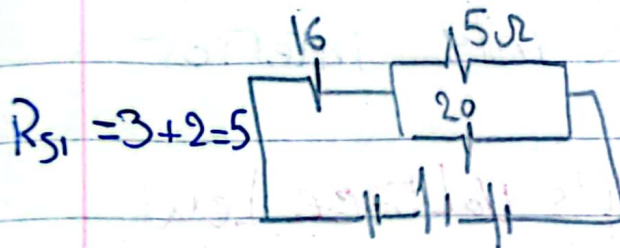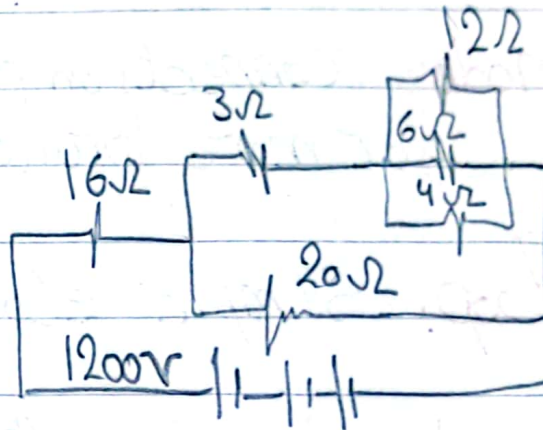

$$\frac{1}{R_{p2}} = \frac{1}{5} + \frac{1}{20} = \frac{1}{4}$$

$$R_2 = 4$$

$$R_t = 16 + 4 = 20\Omega$$

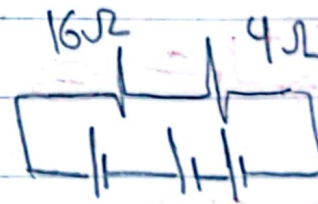

$$I = V/R = 60A$$

**Branch:** is a group of components that carry the same current

**node:** connection point between two or more branches

**Loop:** Simple closed path in circuit

**mesh:** is a loop that doesn't have closed path in its interior


**"K.V.L" Kirchhoff's Voltage Law**

$$\sum V \uparrow = 0 \text{ Rise} \quad \sum V \downarrow = 0 \text{ Fall}$$


$$\sum V \uparrow = \sum V \downarrow = 0$$



V Fall

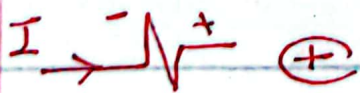

V Rise

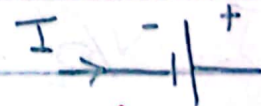

لو ما شئ معاكها -

لو ما شئ ضدكها +



(فرد)

(مزد)


\* لو مس می بیند افترض اشارة المقاومة بالسالب



$$+V_1 - IR_1 - IR_2$$


$$-V_2 - IR_3 - IR_4$$

$$+V_3 + IR_5 + V_4 = 0$$

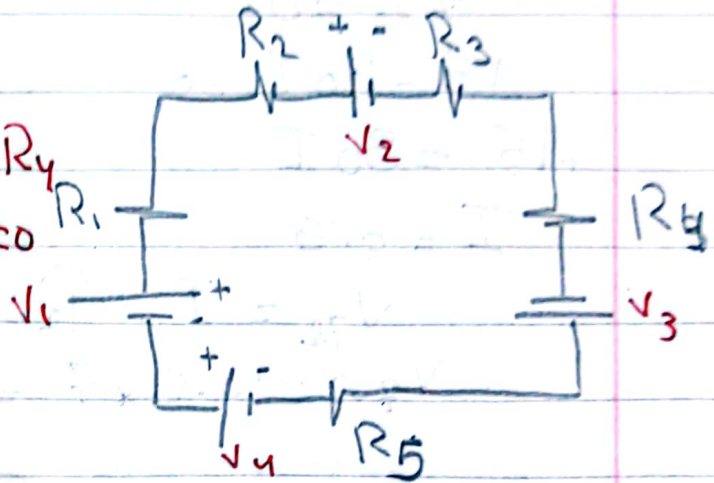

$$E_1 + I_1 R_1 + I_1 R_3 = 0$$

$$+ I_2 R_2 - E_2 + I_2 R_3 = 0$$

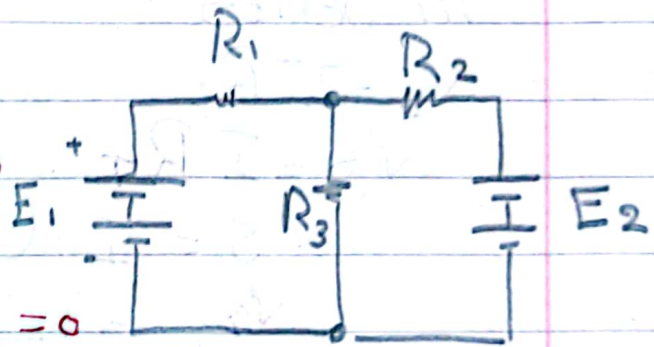

$$\begin{aligned}
 +40 - 6I - 7I \\
 - 8I - 25 - 5I \\
 - 4I = 0
 \end{aligned}$$


$$15 - 30I = 0$$

$$+15 = 30I$$

$$I = 0.5$$

$$V_{7\Omega} = I \times R$$

$$V_{7\Omega} = 0.5 \times 7 = 3.5V$$

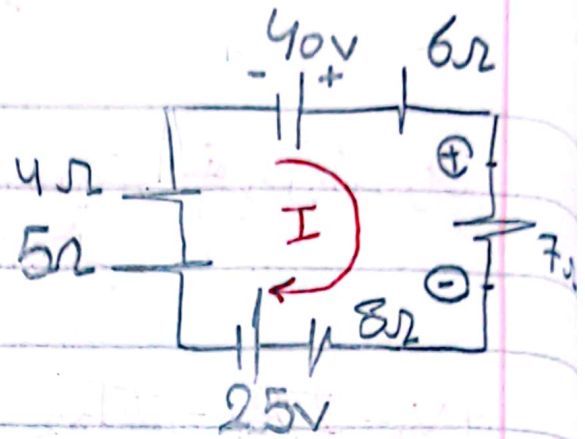

### Voltage Division

in Series

$$V_2 = I R_2$$


$$V_S = I R_T$$

$$V_S = I (R_1 + R_2 + R_3)$$

$$\frac{V_2}{V_S} = \frac{I R_2}{I (R_1 + R_2 + R_3)}$$

$$\Rightarrow V_2 = \frac{R_2}{R_1 + R_2 + R_3} \times V_S$$
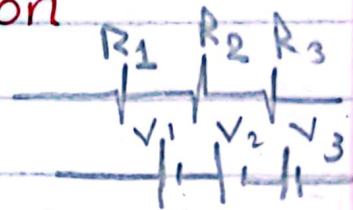
$$\Rightarrow V_x = \frac{R_x}{R_T} V_S$$



## EXAMPLES

How much current will flow through a 2-Ω resistor connected in series with a 4-Ω resistor, and the combination connected across a 12-V source? What is the voltage across each resistor?

$$V_1 = V \frac{R_1}{R_1 + R_2} = 12 \frac{2}{2+4} = 4 \text{ V} \quad V_2 = V \frac{R_2}{R_1 + R_2} = 12 \frac{4}{2+4} = 8 \text{ V}$$

○ 6

1  
6



## EXAMPLES

- Find  $V_3$  and its polarity if the current  $I$  in the circuit of the Figure is  $0.40\text{ A}$ .

Assume that  $V_3$  has the same polarity as  $V_1$ . Applying KVL and starting from the lower left corner.

$$V_1 - I(5.0) - V_2 - I(20.0) + V_3 = 0$$

$$50.0 - 2.0 - 10.0 - 8.0 + V_3 = 0$$

$$V_3 = -30.0\text{ V}$$

Terminal  $b$  is positive with respect to terminal  $a$ .

