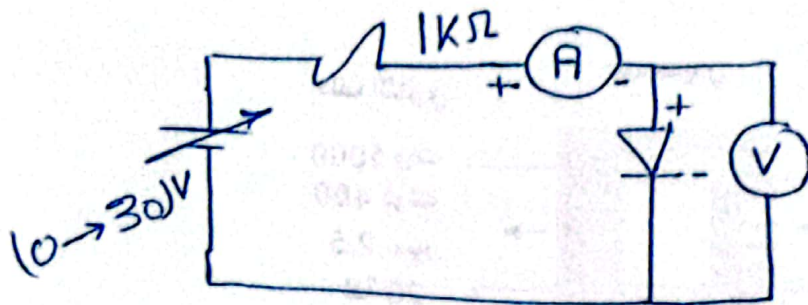


Experiment 1


الاسم (Name) / V-I characteristics of diode

الهدف (Purpose) / reaction between
(Aim)

Voltage and Current in Diodes
by applying voltage across it
and measuring the current through
it



Forward
Biased

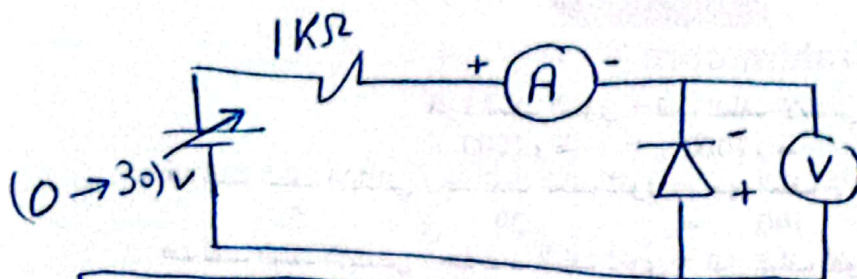

Reverse
Biased


V_{AK}	$I (mA)$
0.1	0
0.2	0
0.3	0
0.4	0
0.5	0
0.6	1.5
0.7	8.8

Forward Biased

V_{AK}	$I (mA)$
-10	1
-15	1.5
-20	2
-25	2.5
-30	3
-35	3.5
-40	4

Reverse Biased

V-I Characteristics of Diode

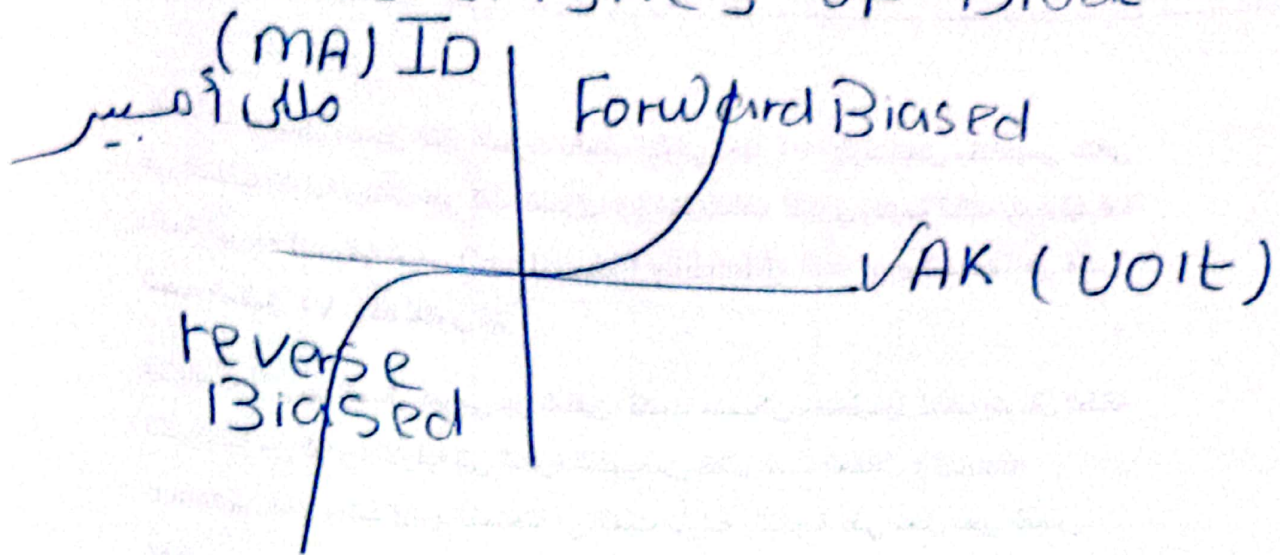



Experiment 2

الاسم / Zener I-V Characteristics


الهدف / ① obtain I-V characteristics of Zener Diode

② study Zener Diode as a voltage regulator

③ Calculate % Line and Load Regulation

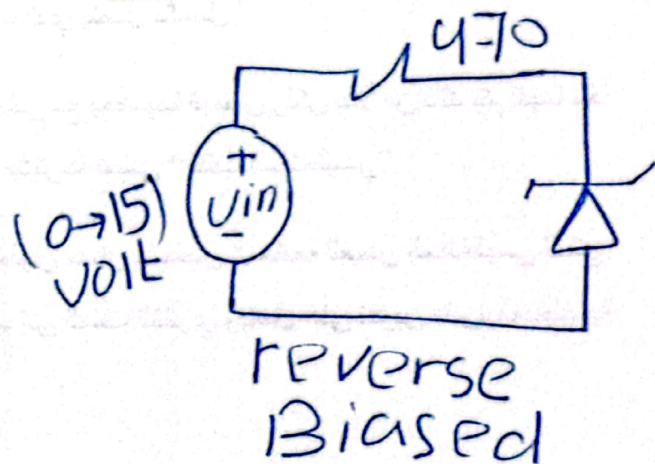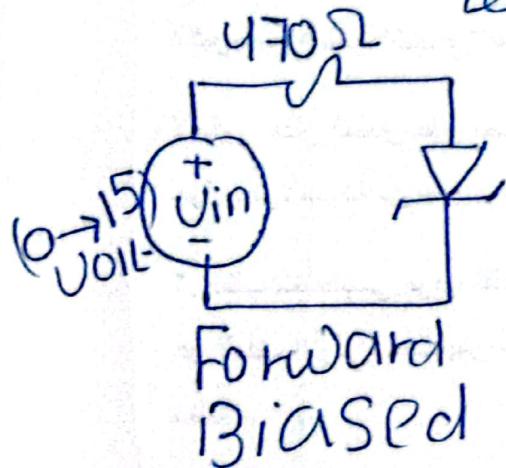

V_Z	I_Z
1 V	0 mA
2 V	0 mA
3 V	0 mA
4 V	0 mA
5.09 V	2.12 mA
5.15 V	5 mA
6	7 mA

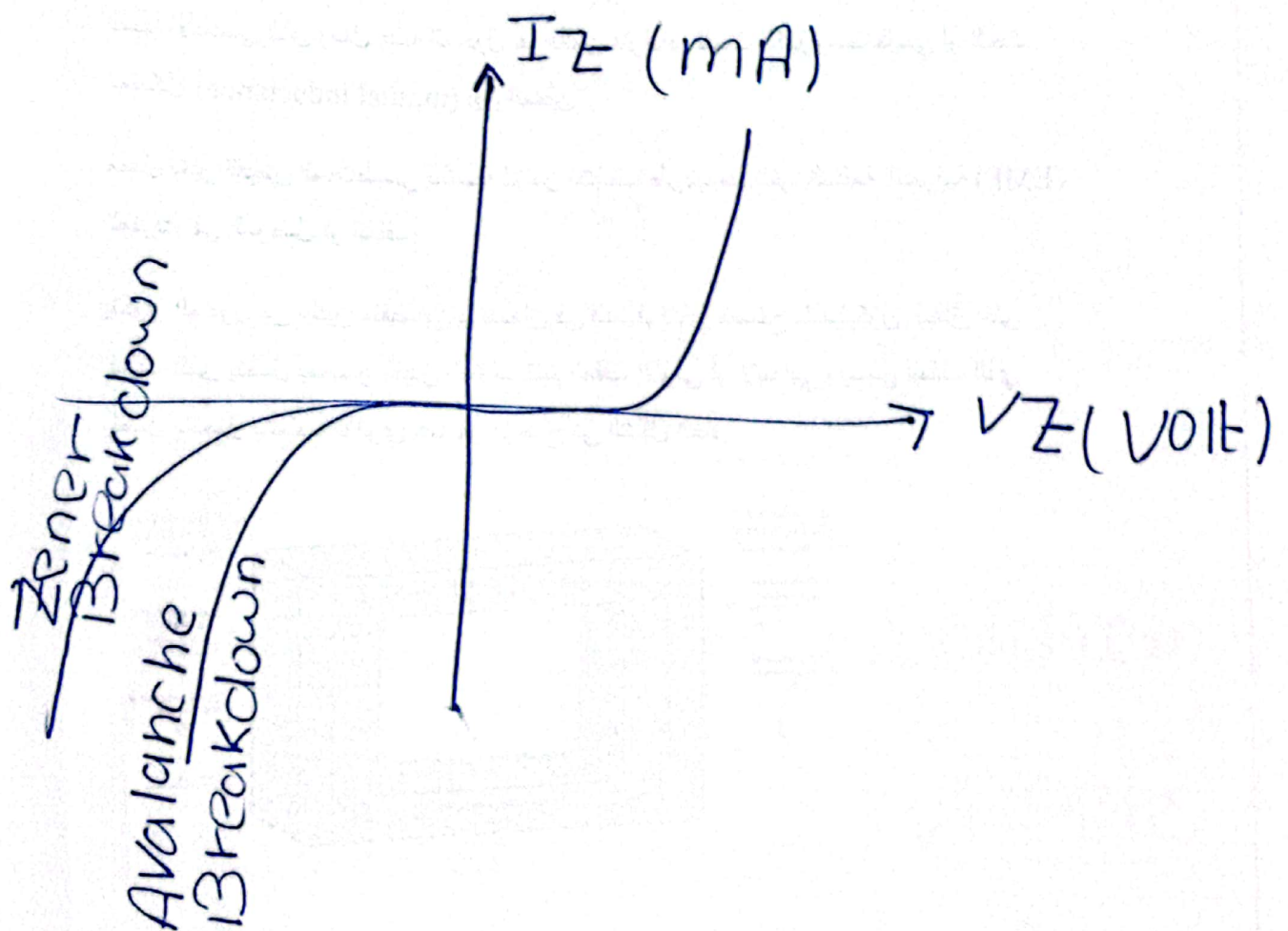


EXPriment(3)

الاسم / Rectifier Circuits

الهدف / * operation of 3 different diode rectifier circuits :-

- ① Half wave Rectifier
- ② Center tapped Full wave Rectifier
- ③ Bridge Full wave Rectifier

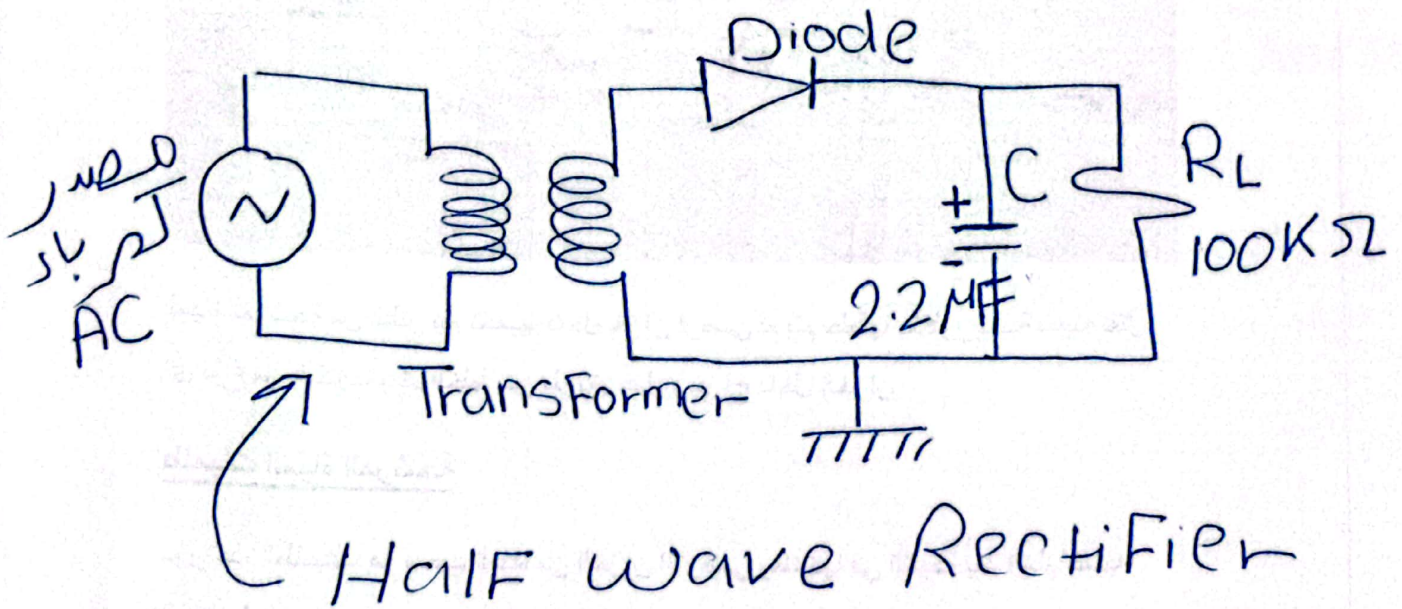* operation of Capacitor Filter
Connected to output of rectifier



$$V_{dc} = V_{oPeak} - \frac{V_{ripple}}{2}$$

$$V_{ripple} = \frac{V_{oPeak}}{F R_L C}$$

$$V_{OPeak} = \sqrt{2} \times V_{o.r.m.s}$$


$$= \sqrt{2} \times 12 \text{ Volt}$$

$$R_L = 100 \times 10^3 \Omega$$

$$C = 2.2 \times 10^{-6} \text{ F}$$

$$F = 50 \text{ Hz}$$

Full wave Rectifier (center tapped)

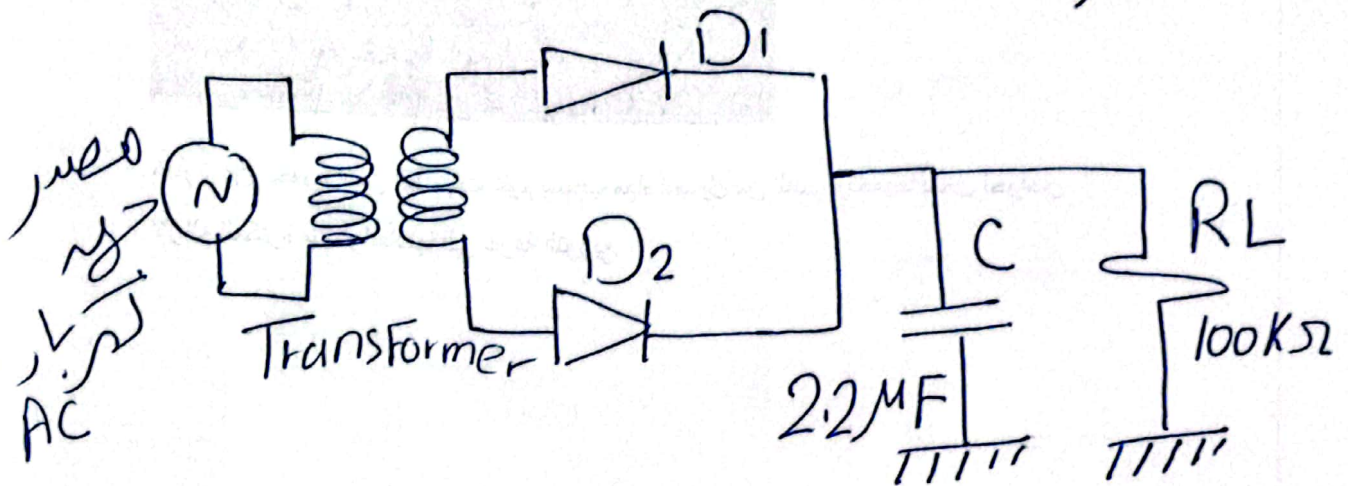

$$V_{dc} = V_{OPeak} - \frac{V_{ripple}}{2}$$

$$V_{ripple} = \frac{V_{OPeak}}{2 F R_L C}$$

$$V_{OPeak} = \sqrt{2} \times 12 \text{ Volt}$$

$$F = 50 \text{ Hz}$$

$$R_L = 100 \times 10^3 \Omega$$


$$C = 2.2 \times 10^{-6} \text{ F}$$

Experiment (4)

الاسم / The input & output characteristics of Common Emitter of BJT

الهدف / Study the characteristics of Common Emitter of BJT and How to Control flow of Current.


input characteristic

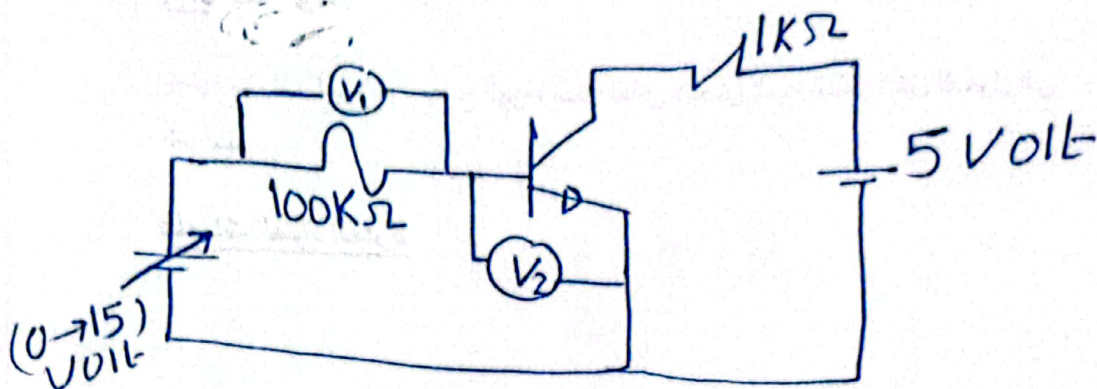

V_{BE} (V_2)	V_B ($100k\Omega$) (V_1)	I_B
0.55V	0.1V	0.1 μA
0.65V	0.5V	0.5 μA
0.68V	2.4V	2.4 μA
0.71V	7.5V	7.5 μA

$$r_{in} = \frac{\Delta V_{BE}}{\Delta I_B} = \frac{0.65 - 0.55}{(0.5 - 0.1) \times 10^{-6}} = 250 \text{ } \Omega$$

Output Characteristic

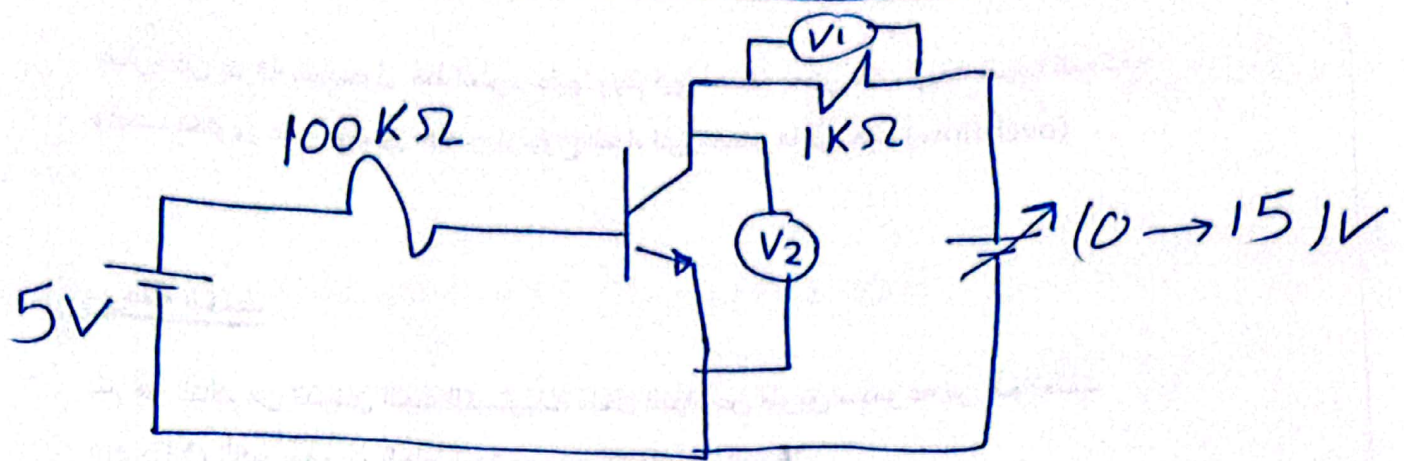

V_{CE} (V_2)	V_1	I_C
0.1V	4V	4mA
0.2V	10V	10mA
0.75V	14V	14mA

المقاومة
الخارجية

$$r_{output} = \frac{\Delta V_{CE}}{\Delta I_C}$$

$$= \frac{0.2 - 0.1}{(10 - 4) \times 10^{-3}}$$

$$= \checkmark \checkmark \Omega$$

Experiment (5)


المسألة / The Common Emitter Amplifier

المسألة 1 / ① Study operation of small signal Common Emitter Amplifier

② Estimate the Factors

that influence the Voltage gain

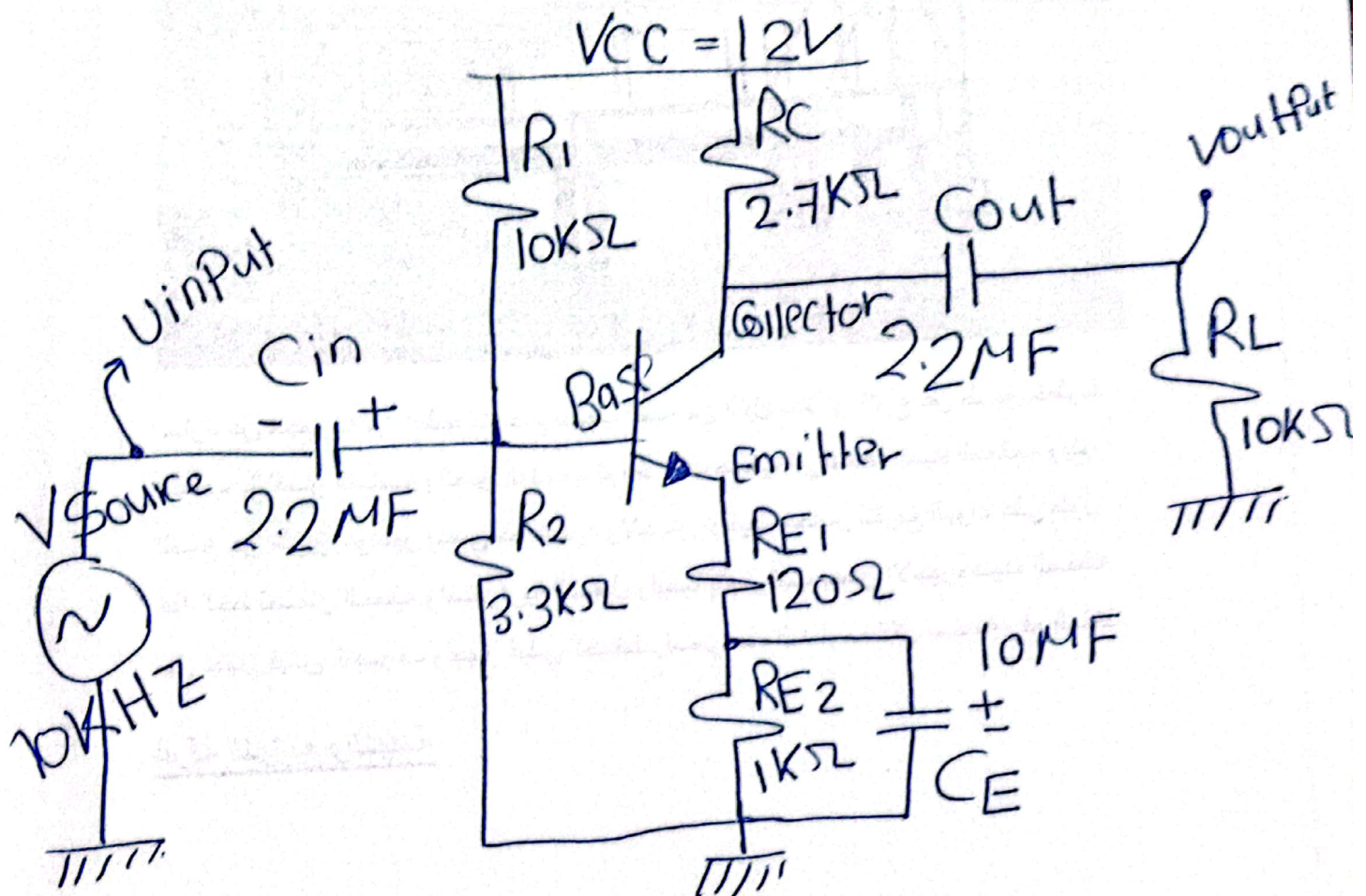③ determine the input and output impedance



V_{in} P-P	V_{out} with R_L	V_{out} without R_L	gain with R_L	gain without R_L
0.1V	1.2V	3V	$\frac{V_{out}}{V_{in}}$ $\frac{1.2}{0.1} = 12$	$\frac{3}{0.1}$ $= 30$