

El-Manzala Higher Institute of Engineering and Technology






Fundamentals of Electrical Engineering

First YEAR

By

Dr. Eman Ahmed Awad Megahed

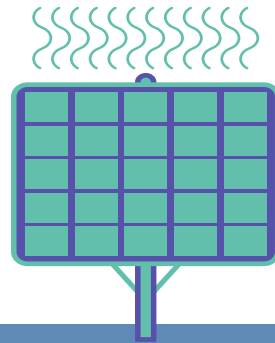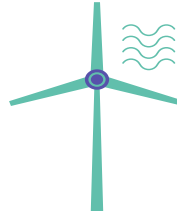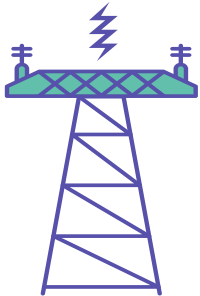


Capacitors and Inductor

Chapter 6

Chapter Content


CH6: Capacitors and Inductor

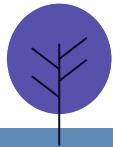- 1 Capacitors and Capacitance**
- 2 Total Capacitance**
- 3 Inductance and Inductor Construction**
- 4 Total Inductance**



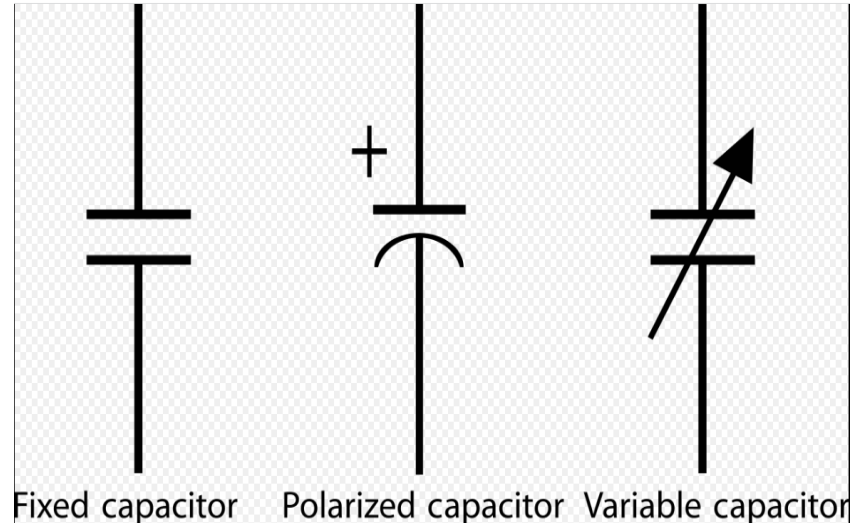1. Capacitors and Capacitance

- ❑ A **capacitor** consists of **two conductors separated by an insulator**.
- ❑ The chief feature of a capacitor is its ability to **store electric charge**, with negative charge on one of its two conductors and positive charge on the other.
- ❑ Accompanying this charge is energy, which a capacitor can release.




1. Capacitors and Capacitance

- ❑ **Capacitance:** the electrical property of capacitors, is a measure of the ability of a capacitor to store charge on its two conductors.
- ❑ if the potential difference between the two conductors is V volts when there is a positive charge of Q coulombs on one conductor and a negative charge of the same amount on the other, the capacitor has a capacitance of

$$C = Q/V$$

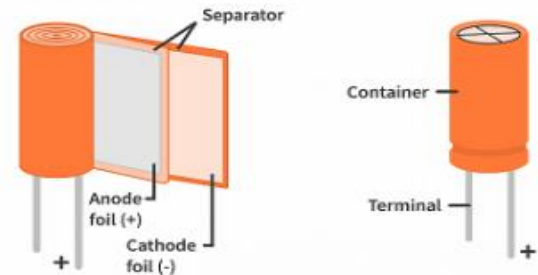where C is the quantity symbol of capacitance



1. Capacitors and Capacitance

EX1 :What is the charge stored on a 2-pF capacitor with 10 V across it'?

SOL:

$$Q = CV = (2 \times 10^{-6})(10) \text{ C} = 20 \mu\text{C}$$


- ❑ The SI unit of capacitance is the farad, with symbol (F).
- ❑ Unfortunately, the farad is much too large a unit for practical applications, and the **microfarad** (pF) and **picofarad** (pF) are much more common.

Milli: 10^{-3}

Micro: 10^{-6}

Nano: 10^{-9}

Pico: 10^{-12}

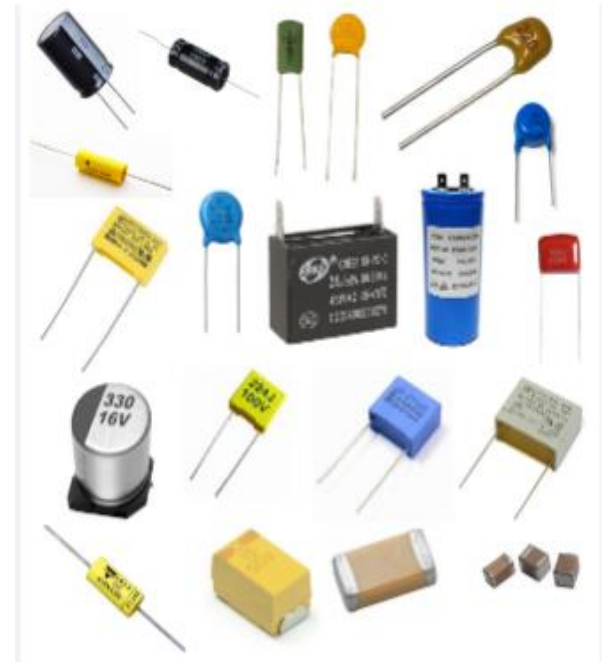


1. Capacitors and Capacitance

- ❑ One common type of capacitor is the **parallel-plate** capacitor.
- ❑ This capacitor has two spaced conducting plates that can be **rectangular**, as shown, but that often are **circular**.
- ❑ The insulator between the plates is called a **dielectric**.
- ❑ For the parallel-plate capacitor, the capacitance in farads is

$$C = \epsilon_0 A/d$$

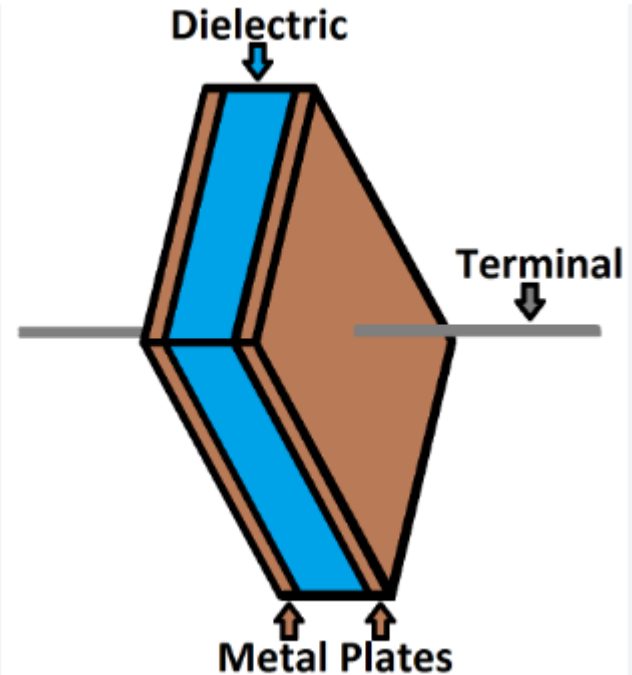- A** is the area of either plate in square meters
d is the separation in meters



1. Capacitors and Capacitance

- ❑ ϵ_0 is the **permittivity** in farads per meter (F/m) of the dielectric.
- ❑ The larger the plate area or the smaller the plate separation, or the greater the dielectric permittivity, the **greater the capacitance**.
- ❑ The permittivity of vacuum, designated by ϵ_0 is 8.85 pF/m.
- ❑ Permittivity of other dielectrics are related to that of vacuum by a factor called the dielectric constant or relative permittivity, designated by ϵ_r
$$\epsilon = \epsilon_0 \epsilon_r$$
- ❑ The dielectric constants of some common dielectrics are 1.0006 for air, 2.5 for paraffined paper, 5 for mica, 7.5 for glass, and 7500 for ceramic.

EX2

EX2: A capacitor has a disk-shaped dielectric of ceramic that has a 0.5-cm diameter and is 0.521 mm thick. The disk is coated on both sides with silver, this coating being the plates. Find the capacitance. (ceramic dielectric constant of 7500)

SOL:

With the ceramic dielectric constant of 7500 in the parallel-plate capacitor formula,

$$C = \epsilon \frac{A}{d} = \frac{7500(8.85 \times 10^{-12})[\pi \times (0.25 \times 10^{-2})^2]}{0.521 \times 10^{-3}} \text{ F} = 2500 \text{ pF}$$

ENERGY STORAGE

The energy stored in a capacitor is:

$$W = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} QV = \frac{1}{2} C V^2$$

where **W** is in joules, **C** is in farads, and **V** is in volts.

❑ Notice that this stored energy does not depend on the capacitor current.

2. TOTAL CAPACITANCE


Parallel Combination

- ❑ The total or equivalent capacitance (C_T or C_{eq}) of parallel capacitors the charge stored in a capacitor is:


$$Q_T = Q_1 + Q_2 + Q_3 \quad \text{but, } Q = CV$$

$$\therefore Q_T = CV_T = CV_1 + CV_2 + CV_3$$

$$\text{or } C_T = C_1 + C_2 + C_3$$

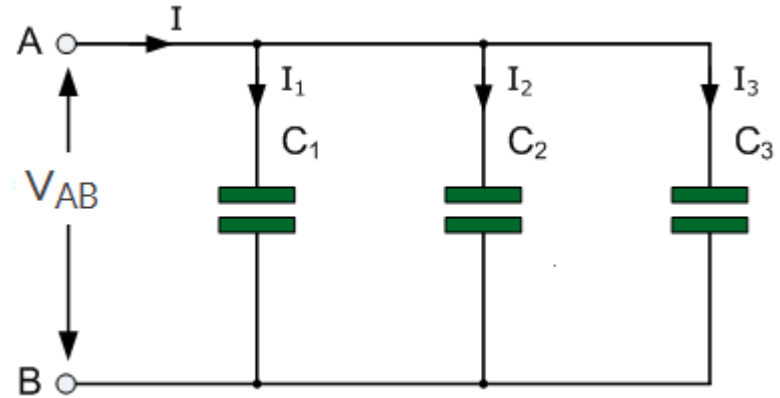

Parallel Combination

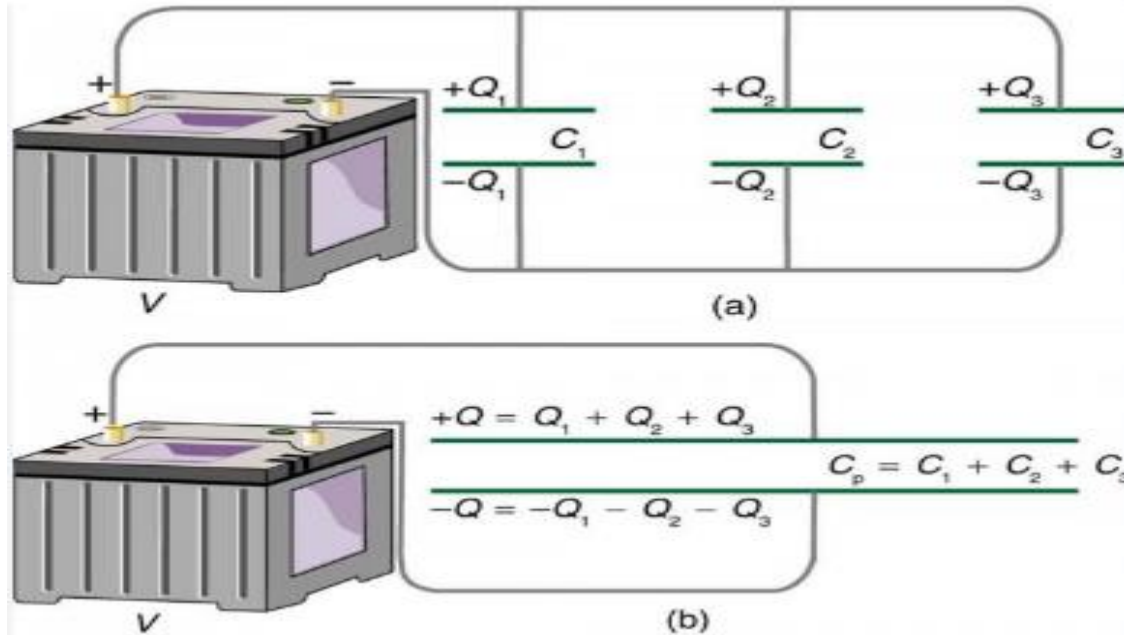

2. TOTAL CAPACITANCE

Series Combination


- ❑ For series capacitors, The Q in each term is the same.
- ❑ The total or equivalent capacitance (C_T or C_{eq}) of series capacitors the charge stored in a capacitor is:

$$V_{AB} = V_{C1} + V_{C2} + V_{C3}$$


$$V_{C1} = \frac{Q_T}{C_1}, \quad V_{C2} = \frac{Q_T}{C_2}, \quad V_{C3} = \frac{Q_T}{C_3}$$

$$V_{AB} = \frac{Q_T}{C_T} = \frac{Q_T}{C_1} + \frac{Q_T}{C_2} + \frac{Q_T}{C_3}$$
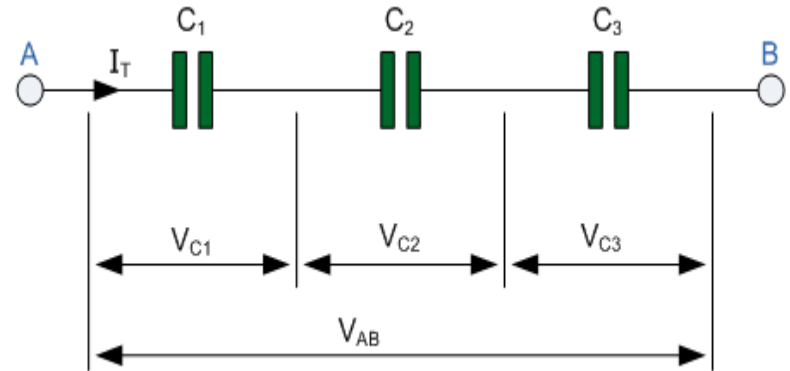
$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \text{etc}$$



Series Combination

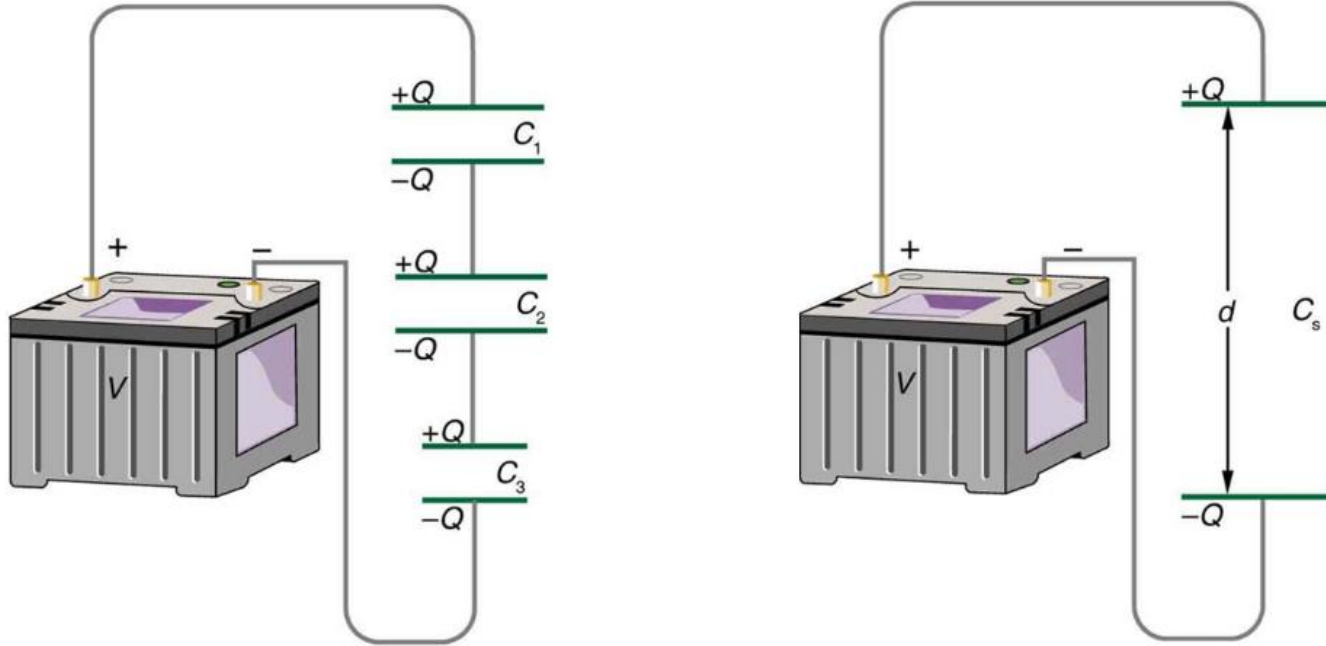

EX3

EX3: What are the different capacitances that can be obtained with a 1- and a 3- μF capacitor?

SOL: The capacitors can produce 1 and 3 μF individually;
 $1 + 3 = 4 \mu\text{F}$ in parallel; and
 $(1 \times 3) / (1 + 3) = 0.75 \mu\text{F}$ in series

EX4

EX4: A 24-V source and two capacitors are connected in series. If one capacitor has 20 μF of capacitance and has 16 V across it, what is the capacitance of the other capacitor?

SOL: By KVL, the other capacitor has $24 - 16 = 8$ V across it.
Also, the charge on it is the same as that
 $Q = C V = (20 \times 10^{-6})(16) \text{ C} = 320 \mu\text{C}$
So, $C = Q / V = 320 \times 10^{-6} / 8 = 40 \mu\text{F}$

End of Lecture 6

