

Question (3):

a)

No.	Parameters	Light emitting diode (LED)	Photo diode
1	function		
2	Schematic symbol		
3	Bias for normal operation		
4	Applications		

Question (4):

- a) Aided with the configurations, sketch a bridge rectifier and demonstrate the output voltage in case of with and without capacitor filter.
- b) An abrupt silicon p-n junction having doping of $N_A = 10^{18} \text{ cm}^{-3}$; $N_D = 10^{15} \text{ cm}^{-3}$ and a circular cross section with diameter of 0.02 inch. Consider $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ for silicon at room temperature, relative permittivity $\epsilon_s = 11.9$ and $\epsilon_o = 8.85 \times 10^{-14} \text{ F/cm}$.


Determine the following:

- i) The value of built in voltage V_o .
- ii) The depletion width in n-region x_{no} .
- iii) The depletion width in p-region x_{po} .
- iv) Total depletion width w_d .
- v) Sketch the electric field intensity E , charge density ρ distributions and potential V across the junction.

Question (5):

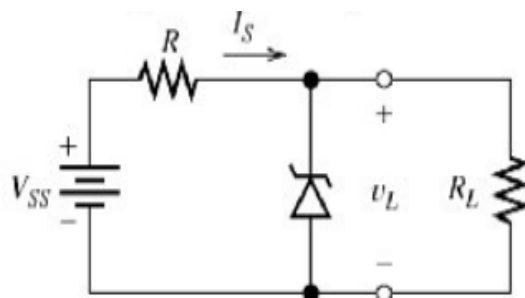- a) Draw the zener diode I-V characteristics and label each region.
- b) Consider a zener diode regulator circuit as shown in Fig. 1.

$V_{SS} = 30 \text{ V}$, $R = 1.5 \text{ k}\Omega$, $R_L = 6 \text{ k}\Omega$ and $V_Z = 10 \text{ V}$. Compute the following:



Fig

- i) The current flowing through the load, I_L
- ii) The source current, I_s
- i) The zener current I_Z at full load.....
- ii) Power of zener diode P_Z
- iii) Power supplied by the source, P_s
- v) Output voltage with removing the zener diode