




Fundamentals of Electrical Engineering



First YEAR


By

Dr. Eman Ahmed Awad Megahed

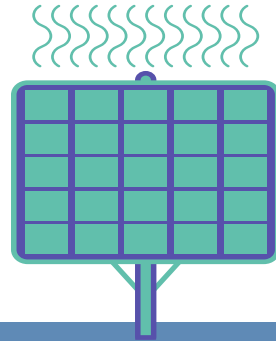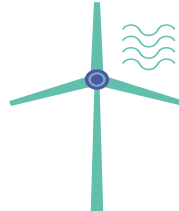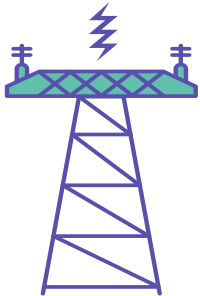

DC Circuit Analysis


Chapter 4

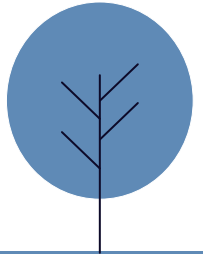

Chapter Content

CH4: DC Circuit Analysis

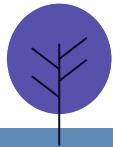
- ☐ KIRCHHOFF'S CURRENT LAW
- ☐ CURRENT DIVISION
- ☐ SOURCE TRANSFORMATIONS
- ☐ MESH ANALYSIS
- ☐ NODAL ANALYSIS



Kirchhoff's law


KCL

Junction or Node Rule

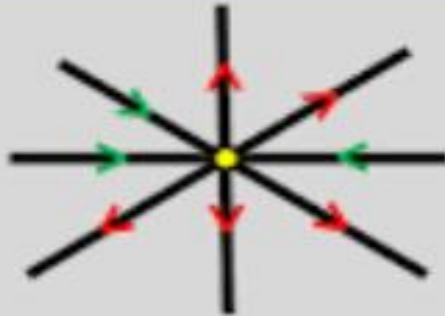

KVL

Mesh and Loop Rule

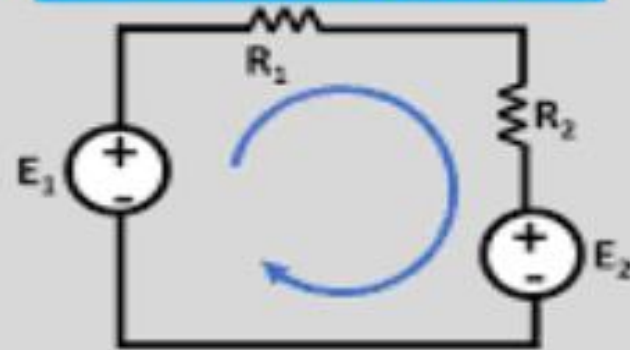


1. KIRCHHOFF'S CURRENT LAW

- ❑ Kirchhoff's Current Law, abbreviated KCL, has three equivalent versions:

At any instant in a circuit,

- ✓ The algebraic sum of the currents leaving a closed surface is zero.
- ✓ The algebraic sum of the currents entering a closed surface is zero.
- ✓ The algebraic sum of the currents entering a closed surface equals the algebraic sum of those leaving.

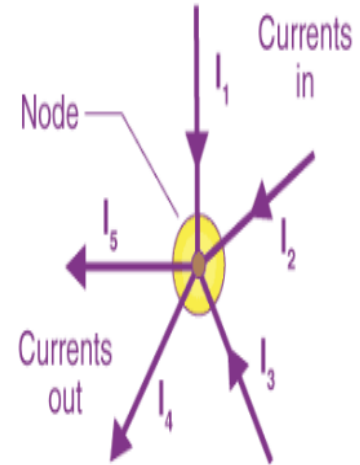
Currents entering the node
equals
current leaving the node



$$I_1 + I_2 + I_3 + (-I_4 - I_5) = 0$$

1. KIRCHHOFF'S CURRENT LAW

- ❑ Remember that: a current entering is a negative current leaving, and that a current leaving is a negative current entering.
- ❑ for a node that has no voltage sources connected the most convenient KCL version is often the third one, restricted such that the currents entering are from current sources and the currents leaving are through resistors.

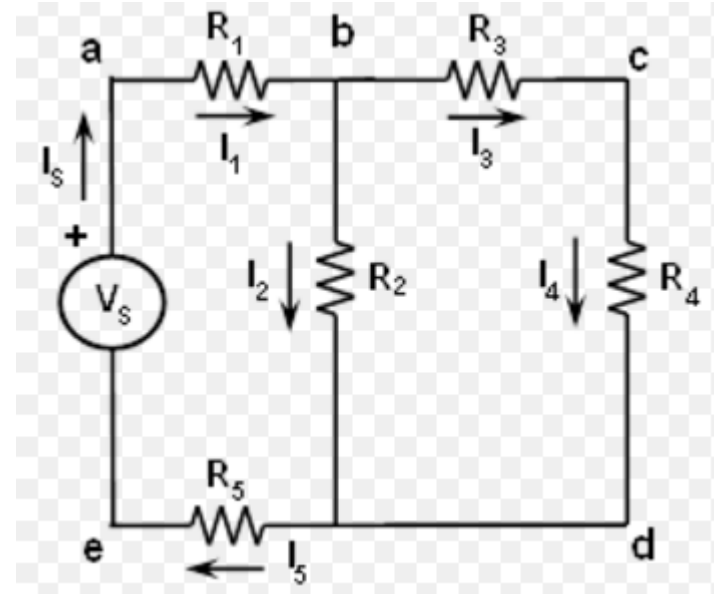

EX1

Find current i_3 at the node shown below.


SOL: Currents i_1 and i_2 are flowing into the node and currents i_3 and i_4 are flowing out of the node. Apply KCL at the given node.

$$i_1 + i_2 = i_3 + i_4$$

Substitute the known quantities

$$2 + 9 = i_3 + 4$$

$$i_3 = 7 \text{ A}$$

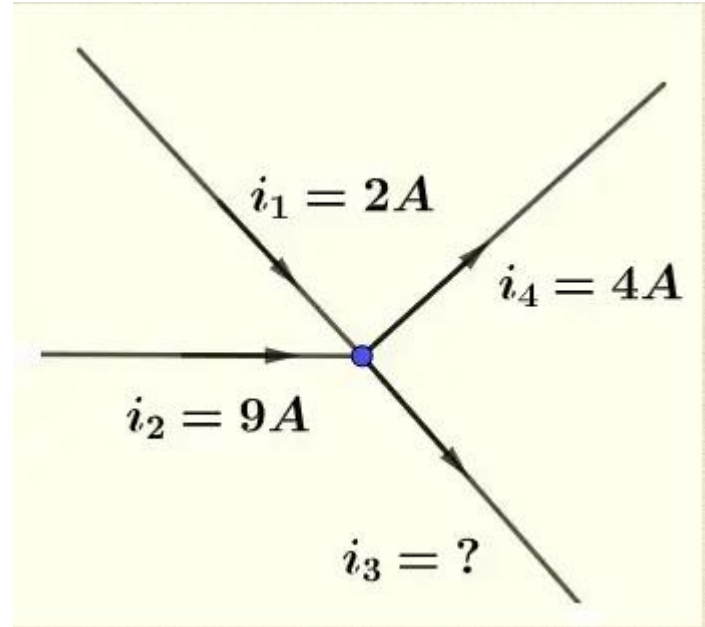

EX2

Determine the current across each resistor and potential difference.

$$\text{KCL at node N1} \quad I_1 + I_2 - I_3 = 0 \quad \text{---(1)}$$

The voltage at node N₁ is V₁, the magnitude of I₁ and I₂ can be determined as

$$I_1 = (20 - V_1)/50 \quad \text{---(2)}$$

$$I_2 = 4 \text{ A} \quad \text{---(3)}$$

$$I_3 = V_1/40 \quad \text{---(4)}$$


Putting the value of I₁, I₂ and I₃ in equation(1), we get

$$I_1 + I_2 - I_3 = 0$$

$$(20 - V_1)/50 + 4 - V_1/40 = 0$$

$$4(20 - V_1) + 800 - 5V_1 = 0$$

$$80 - 4V_1 + 800 - 5V_1 = 0$$

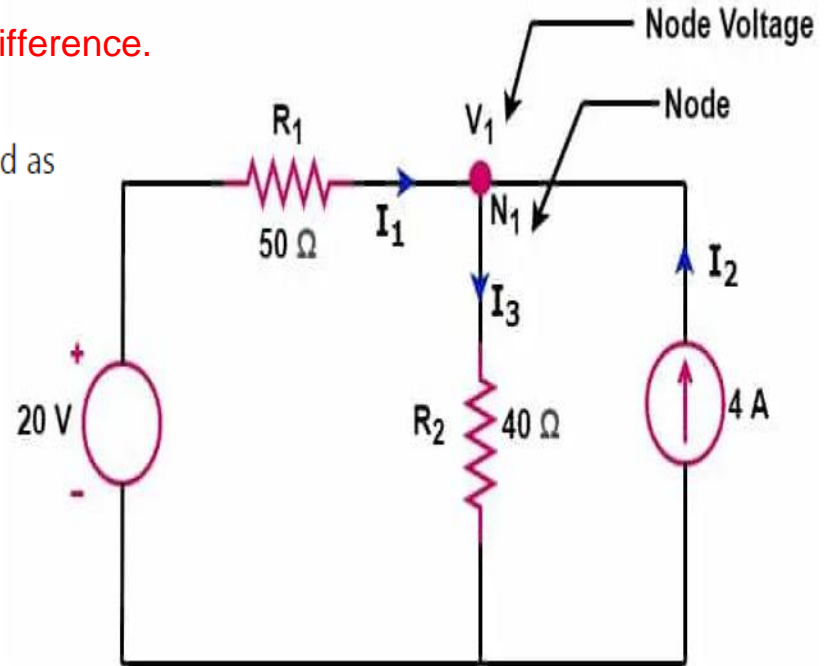

EX2

$$9V_1 = 880$$

$$V_1 = 97.78 \text{ Volts} \text{ —————(5)}$$

Current through Resistance R_1

$$I_1 = (20 - V_1)/50$$


$$I_1 = (20 - 97.78)/50$$

$$= -77.78/50$$

$$\mathbf{I_1 = -1.5556 \text{ A}}$$

Current through Resistance R_2

$$I_3 = V_1/40 = 97.78/40 = \mathbf{2.4445 \text{ A}}$$

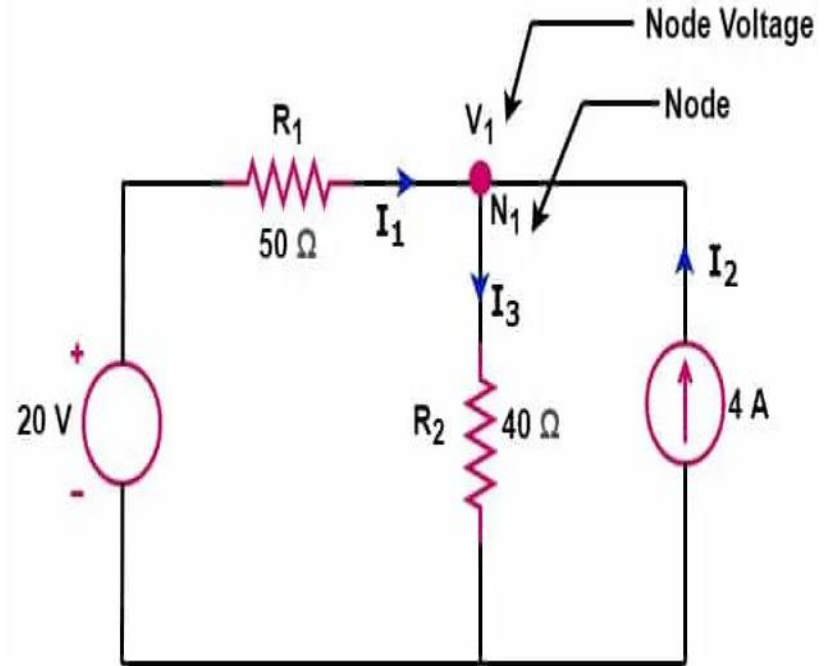


EX2

$I_1 + I_2 = I_3$ (KCL Equation for this circuit)

$$-1.5556 + 4 = 2.4445$$

$$4 = 2.4445 + 1.5556$$

$$4 = 4 \text{ [KCL proved]}$$

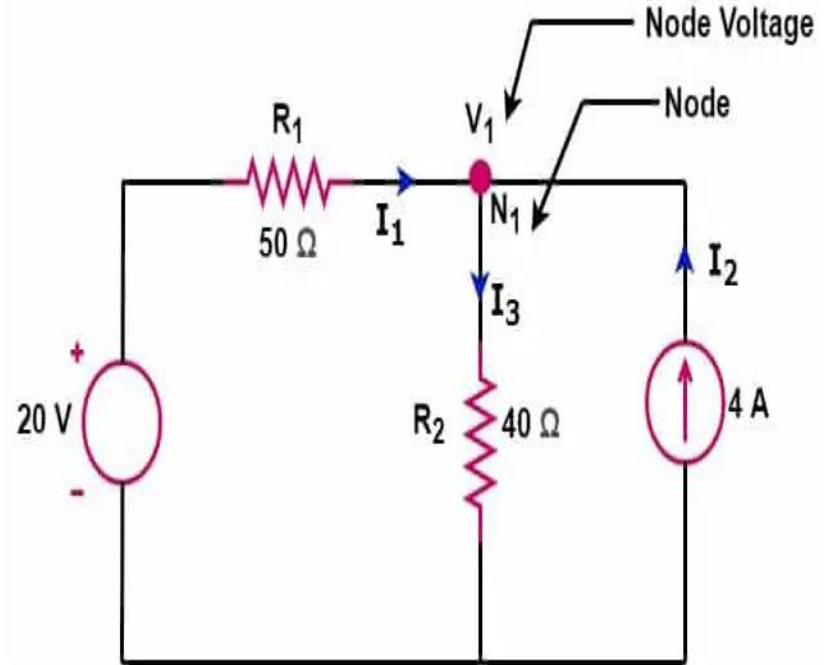

EX3

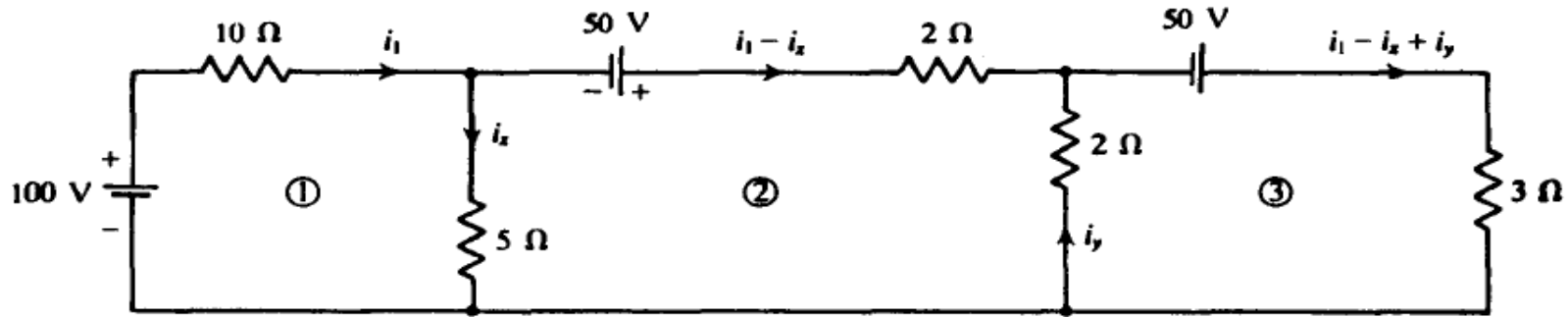


Fig.


Determine the currents i_x and i_y in the network shown in Fig.

| On the basis of KCL, the currents in the remaining branches are also marked in Fig. By KVL for meshes 1, 2, and 3,

$$100 = 10i_1 + 5i_x \quad 50 = 2(i_1 - i_x) - 2i_y - 5i_x \quad 50 = 3(i_1 - i_x + i_y) + 2i_y$$

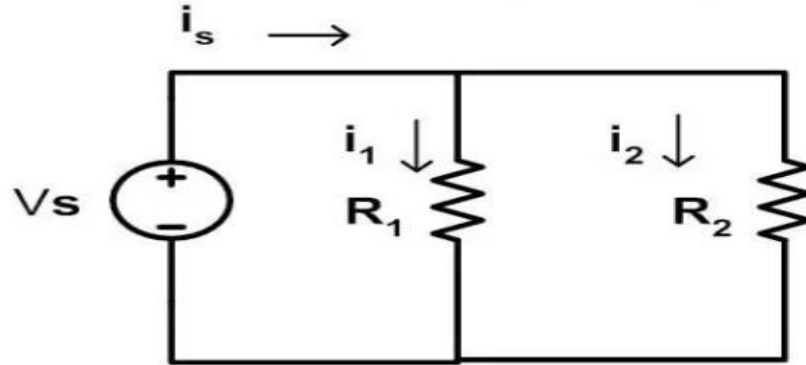2. CURRENT DIVISION

- ❑ The current division or current divider rule applies to resistors in parallel.
- ❑ It gives the current through any resistor into the parallel combination



$$i_1 = \frac{R_2}{R_1 + R_2} i_s$$

$$i_2 = \frac{R_1}{R_1 + R_2} i_s$$

2. CURRENT DIVISION

$$I_1 = \frac{V}{R_1} \quad \text{and} \quad I_2 = \frac{V}{R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2} \dots \dots \dots (2)$$

$$I = \frac{V (R_1 + R_2)}{R_1 R_2} \dots \dots \dots (4)$$

$$I_1 = I \frac{R_2}{R_1 + R_2} \quad \text{and} \quad I_2 = I \frac{R_1}{R_1 + R_2}$$

$$V = I_1 R_1 = I_2 R_2$$


$$I = \frac{I_1 R_1 (R_1 + R_2)}{R_1 R_2} = \frac{I_1}{R_2} (R_1 + R_2)$$

$$I = \frac{I_2 R_2 (R_1 + R_2)}{R_1 R_2} = \frac{I_2}{R_1} (R_1 + R_2)$$

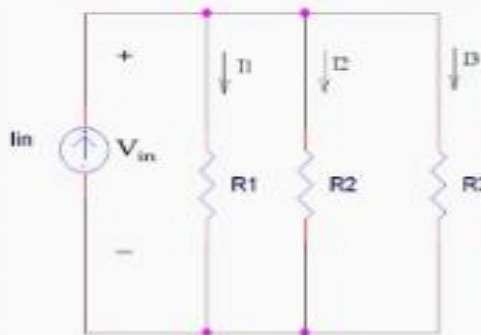2. CURRENT DIVISION

Current Division

All resistors in parallel share the same voltage




The diagram shows a circuit with a voltage source V_{in} on the left, connected in parallel with three resistors: R_1 , R_2 , and R_3 . The total current entering the parallel combination is I_{in} . The current through R_1 is I_1 , through R_2 is I_2 , and through R_3 is I_3 . The voltage across each resistor is V_{in} .

$$I_1 = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} I_{in}$$
$$I_2 = \frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3} I_{in}$$
$$I_3 = \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2} I_{in}$$

Assignment

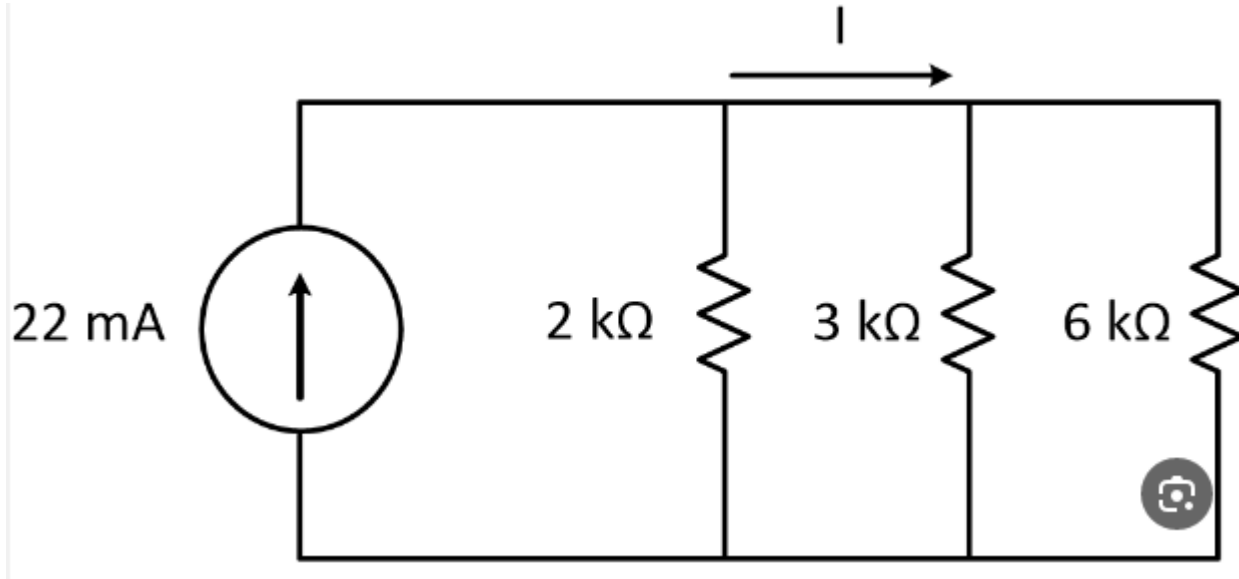
Determine the current across each resistor and potential difference.



3.SOURCE TRANSFORMATIONS

Figure (a) shows the transformation from a voltage source to an equivalent current source.

Figure (b) the transformation from a current source to an equivalent voltage source.

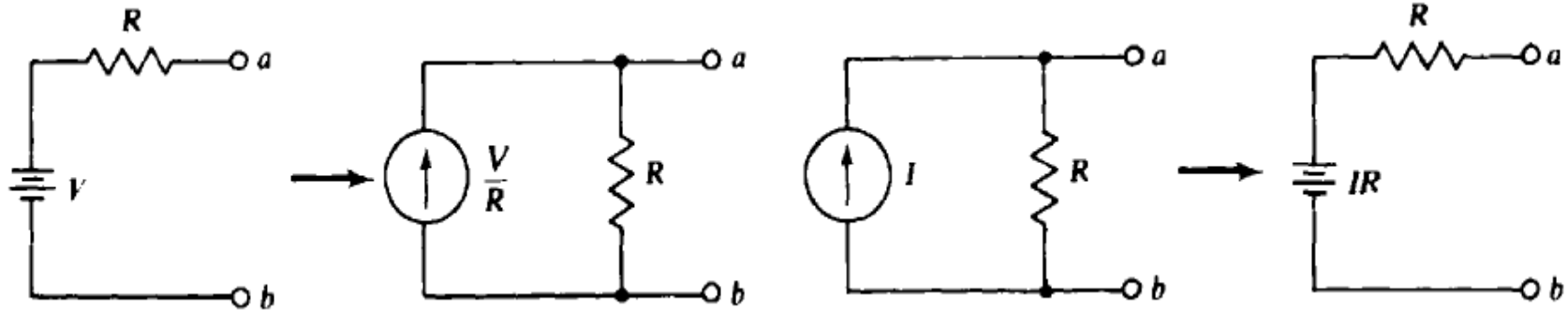


4. MESH ANALYSIS

Mesh analysis is defined as


The method in which the current flowing through a planar circuit is calculated.

$$I_1 R_1 + (I_1 - I_2) R_3 = V_1 - V_3$$
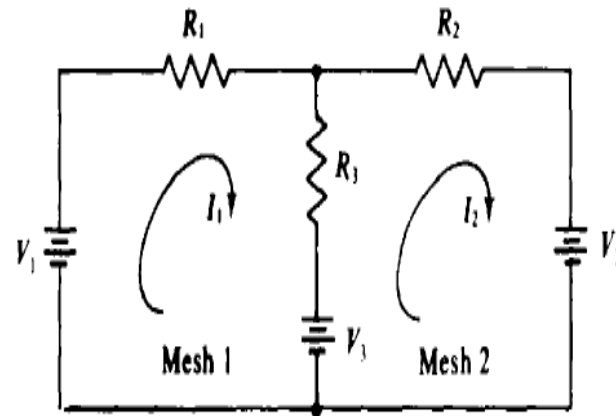
$$-R_3 I_1 + (R_2 + R_3) I_2 = V_3 - V_2$$



(a)

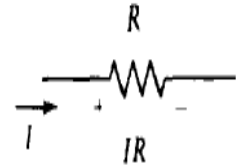

(b)

EX

Example :

In the given circuit 90v is the battery value, 5A is the current source and the three resistors are 9 ohms, 6 ohms, and 8 ohms. Using mesh analysis, determine the current across each resistor and potential difference.

$$90 - I_1 R_1 - R_2(I_1 - I_2) = 0$$


$$90 - 9I_1 - 6(I_1 - I_2) = 0$$

$$-15I_1 + 6I_2 = -90$$

$$5I_1 - 2I_2 = 30 \text{ (this is obtained by dividing the equation with -3)}$$

$$I_1 = 4A$$

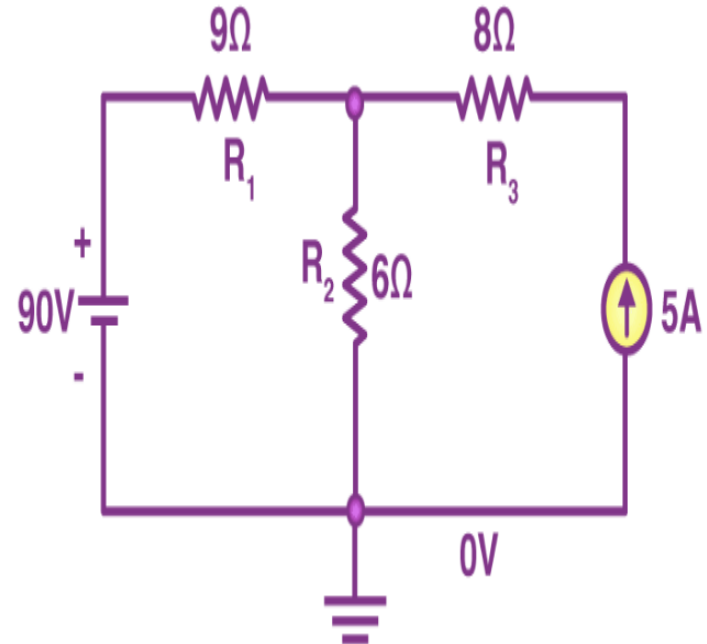So, through R_1 , 4A current is flowing and through R_3 , 5A current is flowing.



EX

Example :

determine the current across each resistor and potential difference.


$$i_1 = I_1, i_2 = -I_2 \text{ and } I_3 = I_1 - I_2$$

$$10 = 50I_1 - 40I_2$$

$$-20 = -40I_1 + 60I_2$$

$$I_1 = -0.143A$$

$$I_2 = -0.429A$$

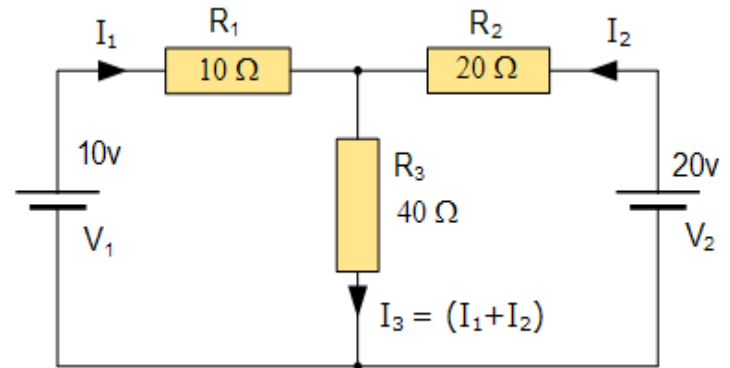

5. NODAL ANALYSIS

Nodal analysis is used for solving any electrical network, and it is defined as The mathematical method for calculating the voltage distribution between the circuit nodes.

This method is also known as the node-voltage method since the node voltages are with respect to the ground. The following are the three laws that define the equation related to the voltage that is measured between each circuit node:

1. Ohm's law
2. Kirchhoff's voltage law
3. Kirchhoff's current law

5. NODAL ANALYSIS

Example 2: Determine the voltage at each node of the given circuit using nodal analysis.

Let node 2 be the reference node, and this node's voltage will be zero.

Using Kirchhoff's current law at each node, we get

$$\frac{V_1}{30} + \frac{V_1 - 100}{5} + \frac{V_1 - V_3}{10} = 0$$

(eq.1)

This is a result of KCL at node 1

$$\frac{V_3 - V_1}{10} + \frac{V_3}{10} + \frac{V_3}{20} = 0$$

(eq.2)


This is a result of KCL at node 3

$$\left(\frac{1}{30} + \frac{1}{5} + \frac{1}{10}\right)V_1 - \left(\frac{1}{10}\right)V_3 = \frac{100}{5}$$
$$-\left(\frac{1}{10}\right)V_1 + \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{20}\right)V_3 = 0$$

Solving the above equations we get

$$V_1 = 68.2\text{v}$$

$$V_3 = 27.3\text{v}$$

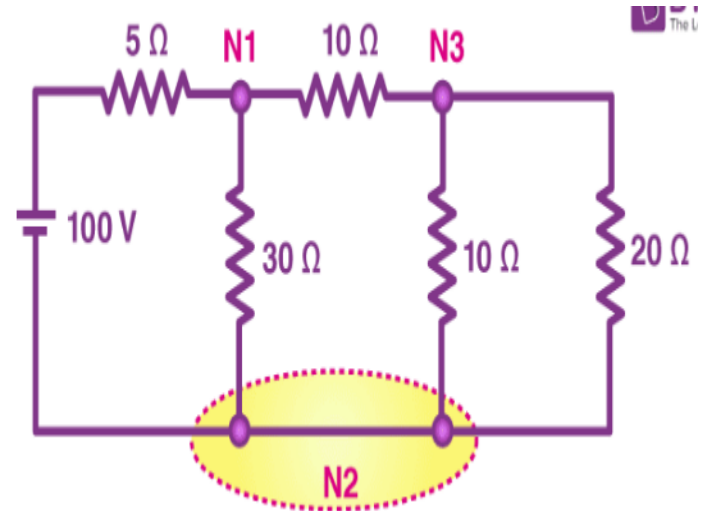

End of Lecture 4

